

The Buck Resonant Converter

- Replacing the switch by the resonant-type switch, to obtain a quasi-resonant PWM buck converter
- It can be shown that there are four modes of operation under the steady-state condition



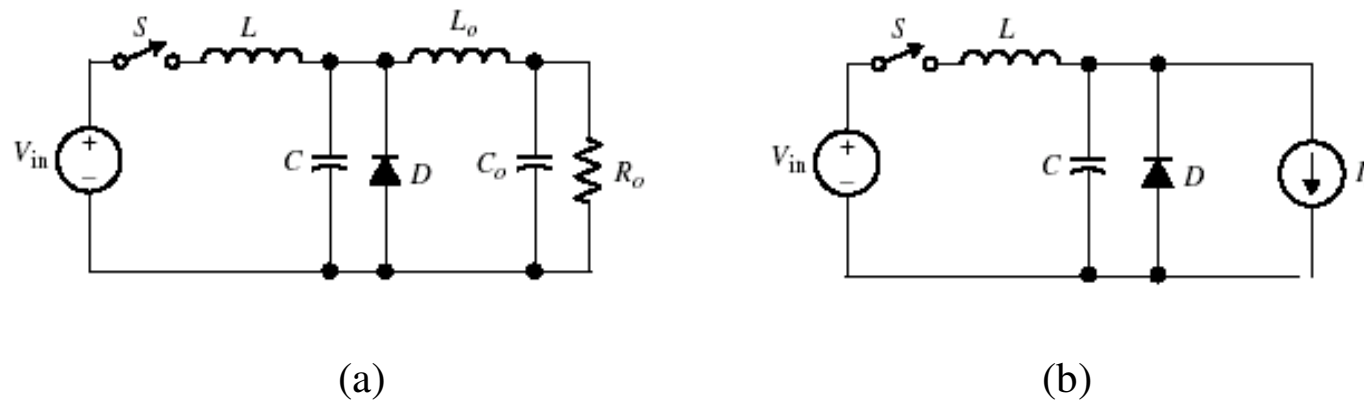


Fig 6.8 (a) Conventional buck converter with L-type resonant switch. (b) Simplified equivalent circuit.


Buck Converter: Equivalent Modes

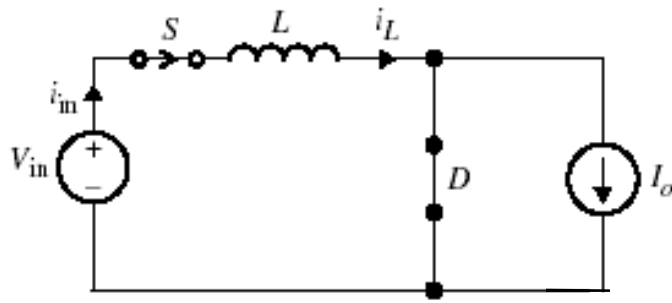


(a)

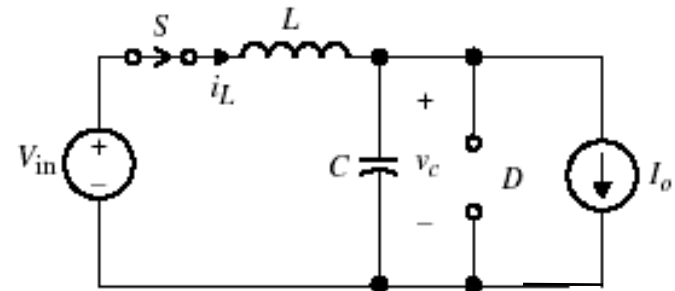

(b)

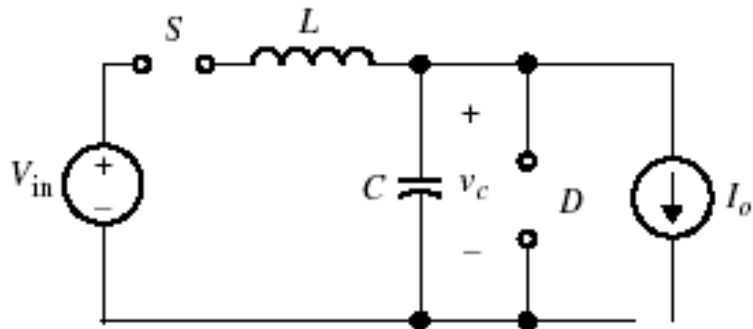

(c)

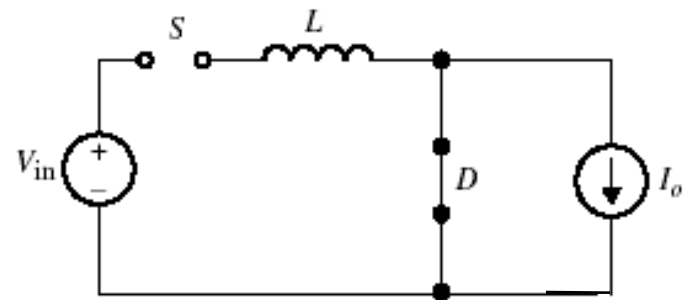

(d)

Fig 6.9 (a) Equivalent circuit for Mode I. (b) Equivalent circuit for mode II. (c) Equivalent circuit for mode III. (d) Equivalent circuit for mode IV.2

Buck Converter: Steady-State Analysis

Mode I [$0 \leq t < t_1$]

- Mode I starts at $t = 0$ when S is turned *ON*
- Assume for $t > 0$, both S and D are *ON*
- The capacitor voltage, v_c , is zero and the input voltage is equal to the inductor voltage

$$V_{in} = L \frac{di_L}{dt}$$

- The inductor current, i_L , is given by

$$i_L(t) = \frac{V_{in}}{L} t$$

- As long as the inductor current is less than I_o , the diode will continue conducting and the capacitor voltage remains at zero.

(6.3)

$$I_o = \frac{V_{in}}{L} t_1$$

- Hence, the time interval $= t_1$ is given by

$$\Delta t_1 = t_1 = \frac{LI_o}{V_{in}} \quad (6.4)$$

- This is the inductor current charging state.

Steady-State Analysis (cont'd)

Mode II [$t_1 \leq t < t_2$]

- Mode II starts at t_1 , diode is open resonant stage between L and C
- The first-order differential equations that represent this mode are

$$C \frac{dv_c}{dt} = i_L - I_o \quad (6.5a)$$

$$L \frac{di_L}{dt} = V_{in} - v_c \quad (6.5b)$$

- Inductor current is given by

$$\frac{d^2 i_L}{dt^2} + \frac{1}{LC} i_L = \frac{I_o}{LC} \quad (6.6)$$

- The general solution for $i_L(t)$ is given by

$$i_L(t) = A_1 \sin \omega_o (t - t_1) + A_2 \cos \omega_o (t - t_1) + A_3 \quad (6.7)$$

- Resonant angular frequency and constants:

$$\omega_o = \sqrt{\frac{1}{LC}} \quad A_1 = \frac{V_{in}}{L\omega_o}$$

- $A_2 = 0$, $A_3 = I_o$

Steady-State Analysis (cont'd)

Equations i_L and v_c are given by

$$i_L(t) = I_o + \frac{V_{in}}{Z_o} \sin \omega_o(t - t_1) \quad (6.8)$$

$$v_c(t) = V_{in} [1 - \cos \omega_o(t - t_1)] \quad (6.9)$$

$$Z_o = \sqrt{\frac{L}{C}} \text{ is known as the characteristic impedance}$$

The time interval in this mode can be derived at $t = t_2$ by setting $i_L(t_2) = 0$,

$$\begin{aligned} i_L(t_2) &= I_o + \frac{V_{in}}{Z_o} \sin \omega_o(t_2 - t_1) \\ &= 0 \end{aligned} \quad (6.10)$$

therefore,

$$\Delta t_2 = t_2 - t_1 = \frac{1}{\omega_o} \sin^{-1} \frac{-Z_o I_o}{V_{in}} = \frac{1}{\omega_o} \left(\pi + \sin^{-1} \frac{Z_o I_o}{V_{in}} \right) \quad (6.11)$$

Mode III starts at $t = t_2$, when the switch is turned *OFF*.

Steady-State Analysis (cont'd)

Mode III [$t_2 \leq t < t_3$]:

At t_2 , the inductor current becomes zero, and the capacitor linearly discharges from $V_c(t_2)$ to zero during t_2 to t_3 .

The capacitor current equals to I_o as given by,

$$i_c = C \frac{dv_c}{dt} = -I_o \quad (6.12)$$

The capacitor voltage $v_c(t)$ is obtained from Eq. (6.12) from t_2 to t_3 with $V_c(t_2)$ as the initial value,

$$v_c(t) = \frac{-I_o}{C}(t - t_2) + V_c(t_2) \quad (6.13)$$

The initial value $V_c(t_2)$ is obtained from previous mode,

$$V_c(t_2) = V_{in} [1 - \cos \omega_o(t_2 - t_1)] \quad (6.14)$$

Substituting Eq. (6.14) into Eq. (6.13),

$$v_c(t) = \frac{-I_o}{C}(t - t_2) + V_{in} [1 - \cos \omega(t_2 - t_1)] \quad (6.15)$$

At $t = t_3$, the capacitor voltage becomes zero,

$$\Delta t_3 = t_3 - t_2 = \frac{C}{I_o} V_{in} [1 - \cos \omega_o(t_2 - t_1)] \quad (6.16)$$

At this point, the diode turns *ON* and the circuit enters Mode IV.

Mode IV [$t_3 \leq t < t_4$]: Steady-State Analysis (cont'd)

At this mode the switch remains *OFF*, but the diode starts conducting at $t = t_3$. Mode IV continues as long as the switch is *OFF*, and the output current starts the free-wheeling stage through the diode.

Initial conditions

$$i_l(t) = 0$$

$$v_c(t) = 0$$

By turning *ON* the switch at $t = T_s$, the cycle repeats these four modes. The time Δt_4 is given by,

$$\Delta t_4 = T_s - \Delta t_1 - \Delta t_2 - \Delta t_3 \quad (6.17)$$

Typical Steady-State Waveforms

Voltage Gain

The expression for the voltage gain, $M = \frac{V_o}{V_{in}}$

Figure 6.10 shows the steady state waveforms for v_c and i_L for the buck converter with L-type switch.

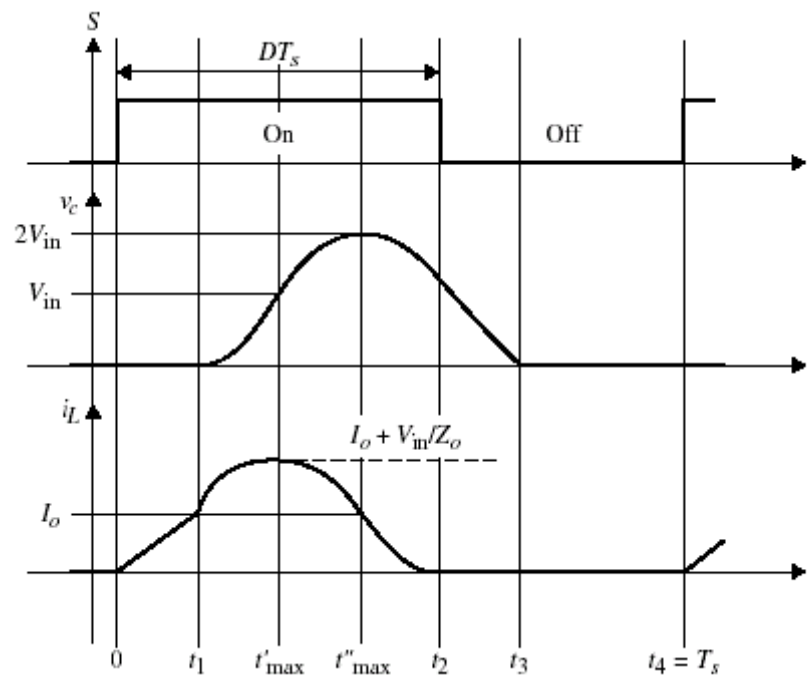


Fig 6.10 Steady-state current and voltage waveforms of buck L-type

Voltage Gain – 1st method

Substitute for $v_c(t)$ from intervals (t_2-t_1) and (t_3-t_2) , to yield,

$$V_o = \frac{1}{T_s} \left[\int_{t_1}^{t_2} V_{in} (1 - \cos \omega_o (t - t_1)) dt + \int_{t_2}^{t_3} \left(\frac{-I_o}{C} (t - t_2) + V_c(t_2) \right) dt \right] \quad (6.18)$$

The voltage gain ratio is given by,

$$\frac{V_o}{V_{in}} = \frac{1}{T_s} \left[(t_2 - t_1) - \frac{\sin \omega_o (t_2 - t_1)}{\omega_o} - \frac{I_o}{V_{in} C} \frac{(t_3 - t_2)^2}{2} + \frac{V_c(t_2)}{V_{in}} (t_3 - t_2) \right] \quad \text{Book correction (6.19)}$$

Substitute for (t_2-t_1) , (t_3-t_2) and $V_c(t_2)$ from the above modes, a closed form expression for M in terms of the circuit parameters can be obtained.

Voltage Gain – 2nd method

The total input energy over one switching cycle,

$$E_{in} = \int_0^{T_s} i_{in} V_{in} dt \quad (6.20)$$

Since i_{in} is equal to $i_L(t)$, Eq. (6.20) is rewritten as,

$$E_{in} = \int_0^{t_1} i_L(t) V_{in} dt + \int_{t_1}^{t_2} i_L(t) V_{in} dt \quad (6.21)$$

Substituting for $i_L(t)$ from Eqs. (6.2) and (6.8) into the above integrals, Eq. (6.21) becomes,

$$E_{in} = V_{in} \left\{ \frac{V_{in} t_1^2}{2L} + I_o(t_2 - t_1) - \frac{V_{in}}{Z_o \omega_o} [\cos \omega_o(t_2 - t_1) - 1] \right\} \quad (6.22) \text{ *Book correction*}$$

Substituting for $\cos \omega_o(t_2 - t_1) = 1 - \frac{I_o(t_3 - t_2)}{C V_{in}}$ from (6.16)

$$E_{in} = V_{in} \left\{ \frac{t_1}{2} I_o + I_o(t_2 - t_1) + \frac{V_{in}}{Z_o \omega_o} \left[\frac{I_o(t_3 - t_2)}{C V_{in}} \right] \right\} \quad (6.23)$$

with, $Z_o \omega_o = \frac{1}{C}$, Eq. (6.23) becomes,

$$E_{in} = V_{in} I_o \left[\frac{t_1}{2} + (t_2 - t_1) + (t_3 - t_2) \right] \quad (6.24)$$

Voltage Gain (cont'd)

The output energy over one switching cycle is:

$$E_o = \int_0^{T_s} I_o V_o dt = I_o V_o T_s \quad (6.25)$$

Equating the input and output energy expressions

$$I_o V_o T_s = V_{in} I_o \left[\frac{t_1}{2} + (t_2 - t_1) + (t_3 - t_2) \right] \quad (6.26)$$

From Eq. (6.26) the voltage gain is expressed by,

$$\frac{V_o}{V_{in}} = \frac{1}{T_s} \left[\frac{t_1}{2} + (t_2 - t_1) + (t_3 - t_2) \right] \quad (6.27)$$

Substituting for t_1 , $(t_2 - t_1)$ and $(t_3 - t_2)$ from previous equations, the voltage gain becomes

$$\frac{V_o}{V_{in}} = \frac{1}{T_s} \left\{ \frac{L I_o}{2 V_{in}} + \frac{1}{\omega_o} \sin^{-1} \frac{-Z_o I_o}{V_{in}} + \frac{C V_{in}}{I_o} [1 - \cos \omega_o (t_2 - t_1)] \right\} \quad (6.28)$$

Normalization

To simplify and generalize the gain equation, the following normalized parameters are defined:

$$M = \frac{V_o}{V_{in}} \quad \text{normalized output voltage} \quad (6.29a)$$

$$Q = \frac{R_o}{Z_o} \quad \text{normalized load} \quad (6.29b)$$

$$I_o = \frac{V_o}{R_o} \quad \text{average output current} \quad (6.29c)$$

$$f_{ns} = \frac{f_s}{f_o} \quad \text{normalized switching frequency} \quad (6.29d)$$

By substituting Eq. (6.29) into Eq. (6.28), the final voltage gain is simplified into

$$M = \frac{f_{ns}}{2\pi} \left[\frac{M}{2Q} + \alpha + \frac{Q}{M} (1 - \cos\alpha) \right] \quad (6.30)$$

where,

$$\alpha = \sin^{-1} \frac{-M}{Q} \quad (6.31)$$

Buck-Control Characteristic Curve

A plot of the control characteristic curve of M vs. f_{ns} under various normalized loads is given in Fig. 6.11

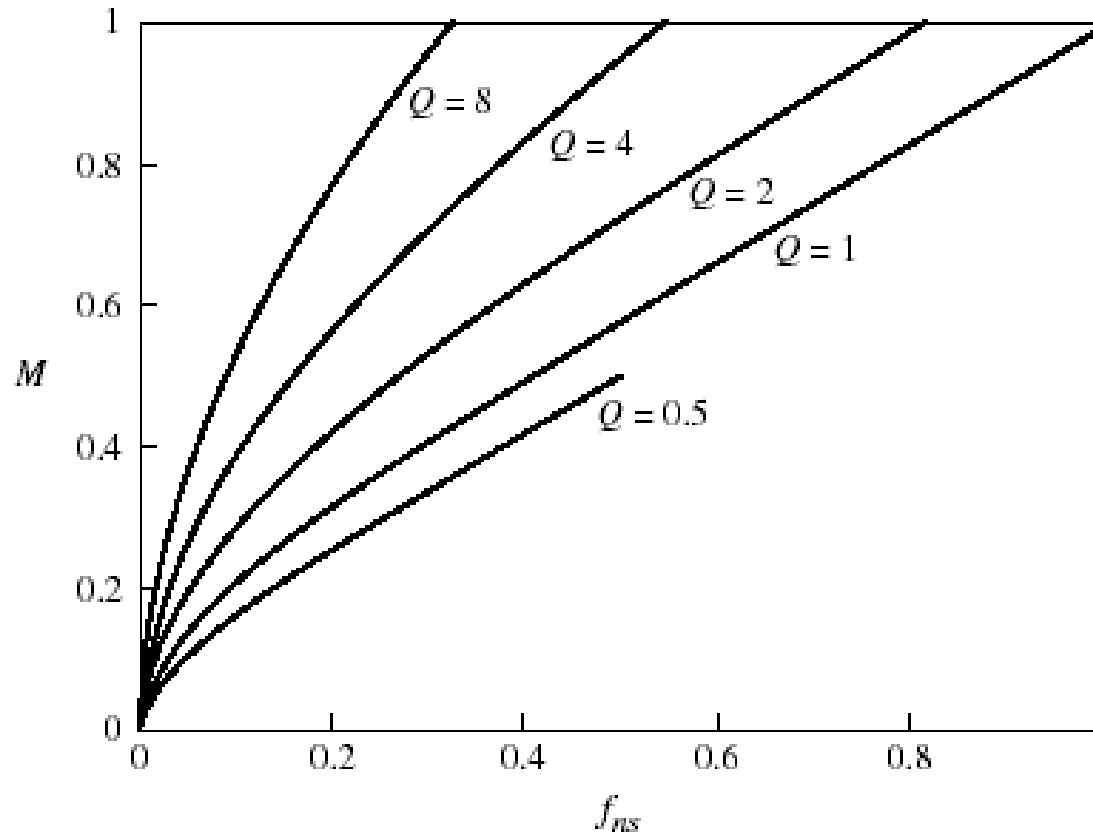


Fig 6.11 Control characteristic curve of M vs. f_{ns} for the ZCS buck converter. 13

ZCS Buck Converter

Example 6.1

Consider the following specifications for a ZCS buck converter of Fig. 6.8(a). Assume the parameters are: $V_{in} = 25V$, $V_o = 12V$, $I_o = 1A$, $f_s = 250kHz$

Design for the resonant tank parameters L and C and calculate the peak inductor current, and peak capacitor voltage. Determine the time interval for each mode.

Solution:

The voltage gain is $M = \frac{V_o}{V_{in}} = \frac{12}{25} = 0.48$. Select $f_{ns} = 0.4$. Determine Q from either the control characteristic curve of Fig. 6.11 or from the gain equation of Eq. (6.30). This results in Q approximately equaling 1. Since $R_o = \frac{V_o}{I_o}$, the characteristic impedance is given by,

$$Z_o = \frac{R_o}{Q} = 12\Omega = \sqrt{\frac{1}{LC}} = 12\Omega \quad (6.32)$$

The second equation in terms of L and C is obtained from f_o . From the normalized switching frequency, f_o may be given by,

$$f_o = \frac{f_s}{f_{ns}}$$

$$f_o = \frac{f_s}{0.4} = 625kHz$$

In terms of the angular frequency, ω_o ,

$$\omega_o = 2\pi f_o = \sqrt{\frac{1}{LC}} \quad (6.33)$$

Solving Eqs. (6.32) and (6.33) for L and C, we obtain,

$$L = \frac{Z_o}{\omega_o} = \frac{12\Omega}{2\pi \times 625 \times 10^3 \text{ rad/sec}}$$

$$= 3.06 \times 10^{-6} \approx 3\mu H$$

$$C = \frac{1}{Z_o \omega_o} = \frac{1}{12 \times 2\pi \times 625 \times 10^3}$$

$$\approx 0.02 \mu F$$

Example 6.1 (cont'd)

The peak inductor current, is given by,

$$I_{l,peak} = I_o + \frac{V_{in}}{Z_o}$$

$$\approx 3 A$$

The peak capacitor voltage is:

$$V_{c,peak} = 2 V_{in}$$

$$= 50 V$$

The time intervals are calculated from the following expressions:

$$t_1 = \frac{I_o L}{V_{in}} = \frac{(1 A) \times (3 \times 10^{-6} H)}{25 V} \approx 0.122 \mu s$$

$$t_2 = t_1 + \frac{1}{\omega_o} \sin^{-1} \left(\frac{-Z_o I_o}{V_{in}} \right)$$

$$\approx 0.122 + \frac{1}{2\pi f_o} \sin^{-1} \left(\frac{-12 \times 1}{25} \right)$$

$$\approx 0.795 \mu s$$

$$t_3 = t_2 + \frac{C V_{in} (1 - \cos \omega_o (t_2 - t_1))}{I_o}$$

$$= 0.795 + \frac{(0.02 \times 25 \times 10^{-6}) (1 - \cos \omega_o 0.67)}{1 A} \approx 1.79 \mu s$$

For t'_{max} we have

$$\omega_o (t'_1 - t_1) = \frac{\pi}{2} \rightarrow t'_1 = \frac{\pi/2}{\omega_o} + t_1$$

$$= 0.4 \mu s + 0.122 \mu s = 0.522 \mu s$$

$$t_4 = 4 \mu s = T_s$$

Exercise 6.2 for practice