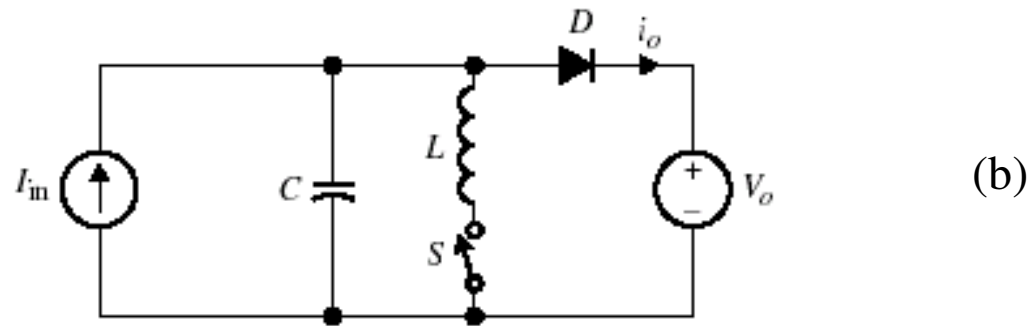
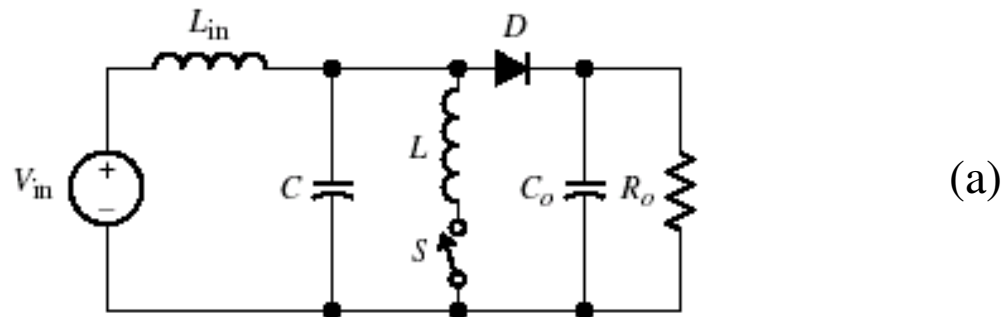



## The ZCS Boost Converter

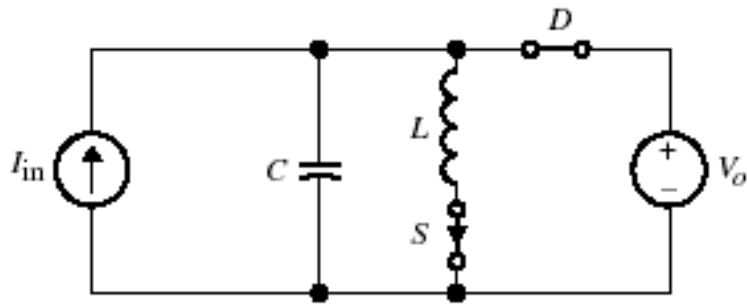The boost-quasi-resonant converter with an M-type switch as shown in Fig. 6.13(a), with its equivalent circuit shown in Fig. 6.13(b).

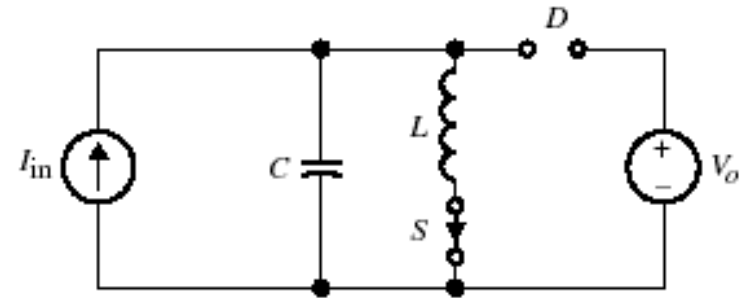


**Fig 6.13** (a) ZCS boost converter with M-type switch. (b) Simplified equivalent circuit.


## ZCS Boost: Equivalent Circuit Modes




(a)



(b)

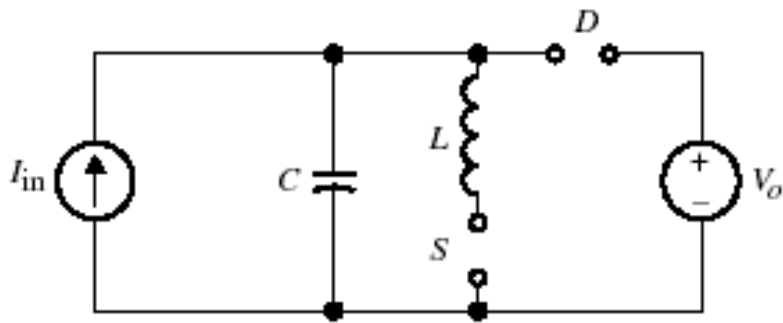

(c)

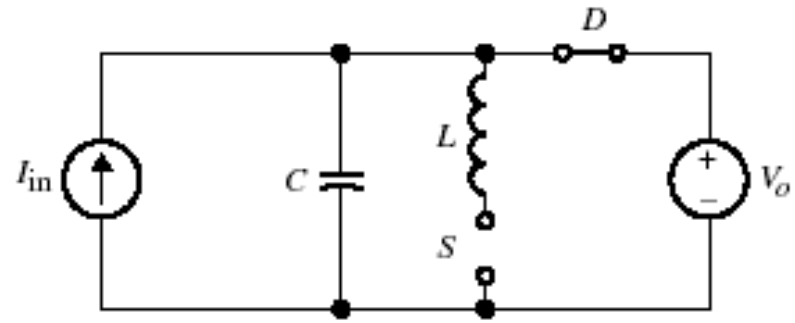

(d)

**Fig 6.14** (a) Equivalent circuit for mode I. (b) Equivalent circuit for mode II. (c) Equivalent circuit for mode III. (d) Equivalent circuit for mode IV.

## ZCS Boost Converter: Steady-State Analysis

### Mode I [ $0 \leq t < t_1$ ]:

Assume switch and the diode are both *ON*

The output voltage is given by

$$V_o = L \frac{di_L}{dt}$$

The initial inductor current and capacitor voltage,

$$i_L(0) = 0 \quad v_c(0) = V_o$$

Integrating Eq. (6.34), the inductor current becomes,

$$i_L(t) = \frac{V_o}{L}t + i_L(0) = \frac{V_o}{L}t$$

When the resonant inductor current reaches the input current,  $I_{in}$ , the diode turns *OFF*,

$$\frac{V_o}{L}t_1 = I_{in}$$

with  $t_1$  given by,

$$t_1 = \frac{I_{in}L}{V_o}$$

At  $t = t_1$ , the diode turns *OFF* since  $i_L = I_{in}$ , and the converter enters Mode II.

## Steady-State Analysis (cont'd)

### Mode II [ $t_1 \leq t < t_2$ ]:

The switch remains closed, but the diode is *OFF* at Mode II as shown in Fig. 6.14(b). This is a resonant mode during which the capacitor voltage starts decreasing resonantly from its initial value of  $V_o$ . When  $i_L = I_{in}$ , the capacitor reaches its negative peak. At  $t = t_2$ ,  $i_L$  equals zero, and the switch turns *OFF*, hence, switching at zero-current.

The initial conditions,

$$v_c(t_1) = V_o \quad i_L(t_1) = I_o$$

From Fig. 6.14(b), the first derivatives for  $i_L$  and  $v_c$  are,

$$L \frac{di_L}{dt} = v_c$$

$$C \frac{dv_c}{dt} = I_{in} - i_L$$

Using the same solution technique used in the buck converter to solve the above differential equations, the expression for  $i_L(t)$

$$i_L(t) = I_{in} + \frac{V_o}{Z_o} \sin \omega_o(t - t_1) \quad (6.37)$$

$$v_c(t) = V_o \cos \omega_o(t - t_1) \quad (6.38)$$

where  $\omega_o = \frac{1}{\sqrt{LC}}$

At,  $t = t_2$   $i_L(t_2) = 0$  and the time interval can be obtained from evaluating Eq. (6.37) at  $t = t_2$  to yield,

$$(t_2 - t_1) = \frac{1}{\omega_o} \sin^{-1} \left( -\frac{I_{in} Z_o}{V_o} \right) = \frac{1}{\omega_o} \left[ \pi + \sin^{-1} \left( \frac{I_{in} Z_o}{V_o} \right) \right] \quad (6.39)$$

## Steady-State Analysis (cont'd)

### Mode III [ $t_2 \leq t < t_3$ ]:

Mode III starts at  $t_2$ , and the switch and the diode are both open as shown in Fig. 6.14(c). Since  $v_c$  is constant, the capacitor starts charging up by the input current source. The capacitor voltage,

$$\begin{aligned} v_c &= \frac{1}{C} \int_{t_2}^t I_{in} dt \\ &= \frac{I_{in}}{C} (t - t_2) + v_c(t_2) \end{aligned} \quad (6.40)$$

The diode begins conducting at  $t = t_3$  when the capacitor voltage is equal to the output voltage, i.e.  $v_c(t_3) = V_o$ .

$$V_o = \frac{I_{in}}{C} (t_3 - t_2) + v_c(t_2)$$

Time interval in this period


$$t_3 - t_2 = \frac{I_{in}}{C} [V_o - v_c(t_2)] \quad (6.41)$$

### Mode IV [ $t_3 \leq t < t_4$ ]:

At  $t_3$ , the capacitor voltage is clamped to the output voltage, and the diode starts conducting again. The cycle of the mode will repeat again at the time of  $T_s$  when S is turned ON again

## ZCS Boost-Typical Steady-State Waveforms

Typical steady state waveforms are shown in Fig. 6.15.

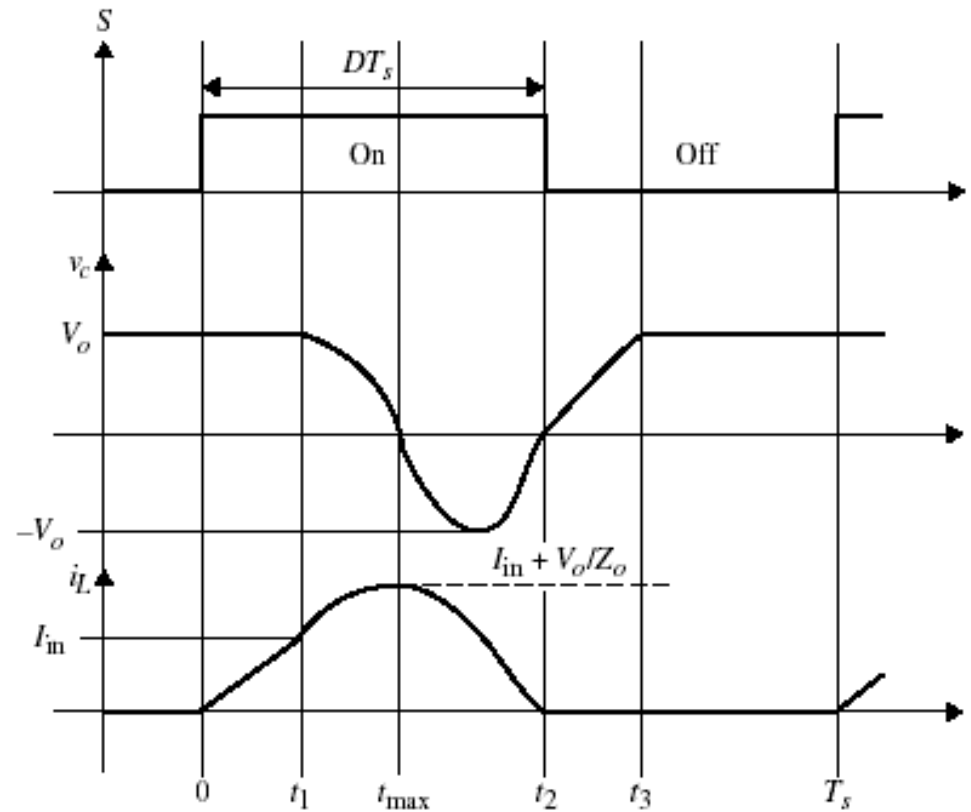

**Fig 6.15** Steady-state waveforms of the boost converter with M-type switch.

## ZCS Boost Converter

### Voltage Gain

Conservation of energy per switching cycle to express the voltage gain,  $M = V_o / V_{in}$

The input energy is,

$$E_{in} = V_{in} I_{in} T_s \quad (6.42)$$

The output energy,

$$E_o = \int_0^{T_s} i_o V_o dt \quad (6.43)$$

The output current equals  $i_o = I_{in} - i_L$  and  $i_o = I_{in}$  for intervals  $0 \leq t \leq t_1$  and  $t_3 \leq t < T_s$ ,

$$E_o = \int_0^{t_1} (I_{in} - i_L) V_o dt + \int_{t_3}^{T_s} I_{in} V_o dt \quad (6.44)$$

The input current is obtained from the conservation of output power as:

$$I_{in} = \frac{V_o^2}{V_{in} R}$$

## ZCS Boost-Voltage Gain

Substituting for the input current and by evaluating Eq. (6.44), the output energy becomes

$$\begin{aligned} E_o &= V_o \int_0^{t_1} \left( I_{in} - \frac{V_o}{L} t \right) dt + I_{in} V_o (T_s - t_3) \\ &= V_o \left( I_{in} t_1 - \frac{1}{2} \frac{V_o}{L} t_1^2 \right) + I_{in} V_o (T_s - t_3) \end{aligned} \quad (6.45)$$

with  $t_1 = \frac{I_{in} L}{V_o}$  and  $(T_s - t_3) = T_s - [t_1 + (t_2 - t_1) + (t_3 - t_2)]$ , and use the equations for  $(t_3 - t_2)$  and  $(t_2 - t_1)$  from Eqs. (6.39) and (6.41), Eq. (6.45) becomes,

$$E_o = -\frac{1}{2} I_{in}^2 L + V_o I_{in} \left[ T_s - \frac{\alpha}{\omega_o} - \frac{C}{I_{in}} V_o (1 - \cos \alpha) \right] \quad (6.46)$$

The voltage gain expression is given by,


$$\frac{M - 1}{M} = \frac{f_{ns}}{2\pi} \left[ \frac{M}{2Q} + \alpha + \frac{Q}{M} (1 - \cos \alpha) \right] \quad (6.47)$$

where,  $\alpha$ ,  $M$ ,  $I_o$  and  $f_{ns}$  are given as before.



## ZCS Boost-Control Characteristic Curve

Fig 6.16 shows the characteristic curve for  $M$  vs.  $f_{ns}$  as a function of the normalized load.

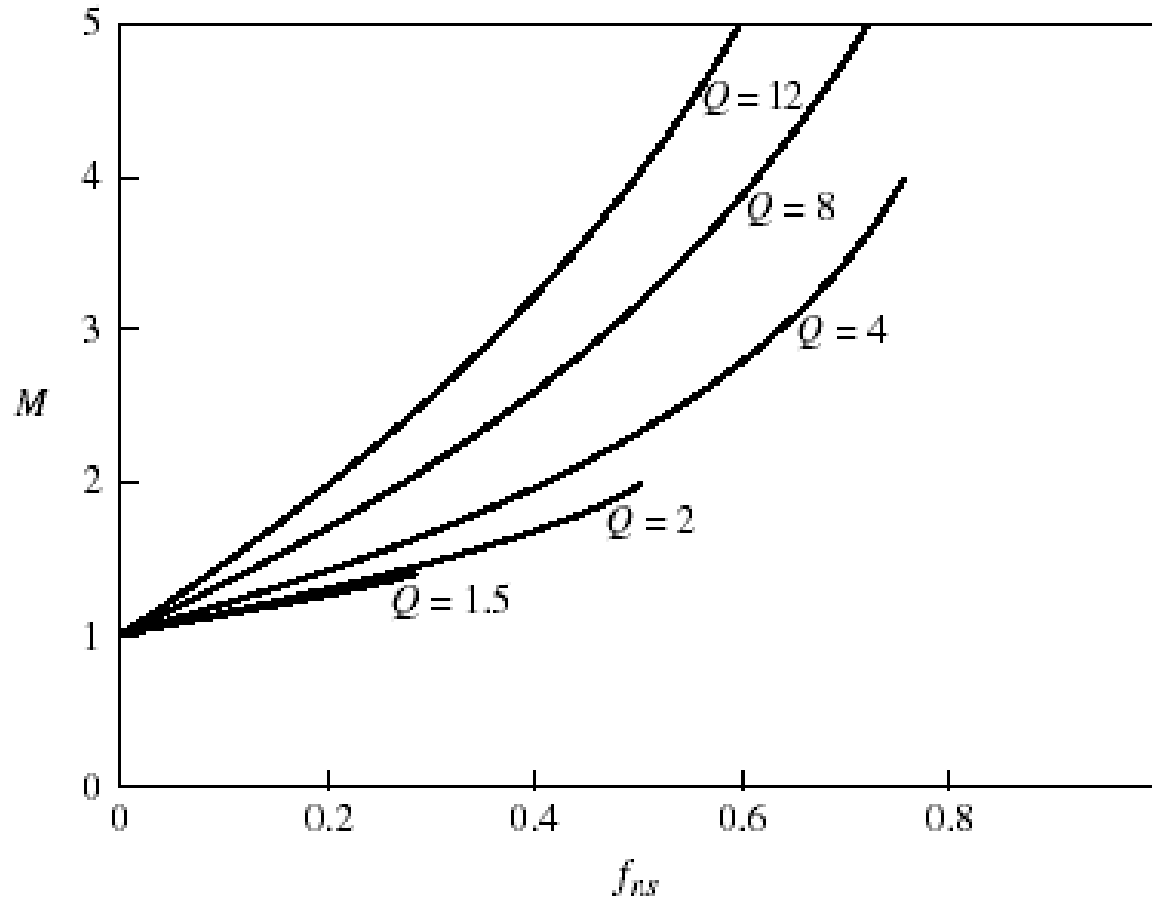

**Fig 6.16** Characteristic curve for  $M$  vs.  $f_{ns}$  for the boost ZCS converter.

## ZCS Boost Converter

### Example 6.2

Design a boost ZCS converter for the following parameters:  $V_{in} = 20V$ ,  $V_o = 40V$ .  $P_o = 20W$ ,  $f_s = 250kHz$ .

**Solution:**

The voltage gain is  $M = \frac{V_o}{V_{in}} = \frac{40}{20} = 2$  Let us select  $f_{ns} = 0.38$ . From the characteristic curve of Fig. 6.16,  $Q$  can be approximated to 6.0

The characteristic impedance is given by,

$$Z_o = \frac{R_o}{Q} = \frac{80\Omega}{6} = 13.33\Omega \quad (6.48)$$

Resonant frequency is,

$$f_o = \frac{f_s}{f_{ns}} = \frac{250kHz}{0.38} = 657.89kHz \quad (6.49)$$

Solve Eqs. (6.48) and (6.49) for L and C

$$L = \frac{Z_o}{2\pi f_o} = \frac{13.33\Omega}{2\pi \times 657.89 \times 10^3} = 3.22 \times 10^{-6} H$$

$$C = \frac{1}{Z_o \omega_o} = \frac{1}{(13.33)(2\pi \times 657.89 \times 10^3)} = 18.14 nF$$

## ZCS Boost Converter

### Example 6.3

Design a boost converter with ZCS, with the following design parameters:  $V_{in}=25V$ ,  $P_0=30W$  at  $I_0=0.5A$ , and  $f_s=100kHz$ . Assume the output voltage ripple  $\Delta V_0$  is 0.2 %

#### Solution:

$$\text{The load resistance, } R = \frac{P_0}{I_0^2} = \frac{30}{(0.5)^2} = 120\Omega$$

$$M = \frac{V_0}{V_s} = \frac{60}{25} = 2.4,$$

From the characteristic curve of Fig. 6.15, approximate Q to 6 when we assume  $f_n = 0.58$ .

$$f_o = \frac{100}{0.58} = 172.4kHz.$$

From Q and  $R_o$ , the characteristic impedance is obtained from,

$$Q = \frac{R_o}{Z_o} = \frac{120}{Z_o} = 6, \text{ and } Z_o = 20 \quad \sqrt{\frac{L}{C}} = 20$$

$$\omega_o = 2\pi(172 \times 10^3) = 1080.7 \times 10^3 \text{ rad / sec}$$

$$\sqrt{\frac{1}{L C}} = 1080.7 \times 10^3$$

Solving for C and L

$$C = 46.27\eta F$$

$$L = 18.51\mu H$$

## Example 6.3 (cont'd)

The time intervals are given by

$$t_1 = \frac{L_r I_i}{V_0} = \frac{18.51 \times 10^{-3} \times 1.2}{60} = 0.370 \mu s$$


$$\begin{aligned} t_2 - t_1 &= \frac{1}{\omega_o} \sin^{-1} \left[ \frac{-Z_0 I_i}{V_0} \right] \\ &= \frac{1}{1080.7 \times 10^3} \sin^{-1} \left[ -\frac{20 \times 1.2}{60} \right] = 3.29 \mu s \end{aligned}$$

$$\begin{aligned} t_3 - t_2 &= \frac{1}{\omega_n} \frac{V_0}{Z_0 I_i} (1 - \cos \alpha) \\ &= \frac{1}{1080.7 \times 10^3} \frac{60}{20 \times 1.2} (1 - \cos 3.553) \\ &= 0.193 \mu s \end{aligned}$$

$$\begin{aligned} t_4 - t_3 &= T - t_1 - (t_{12}) - (t_{23}) \\ &= 10 - 0.370 - 3.29 - 0.193 = 6.147 \mu s \end{aligned}$$

## Other ZCS Boost Converter

Figure 6.17(a) shows the quasi-resonant boost converter by using the L-type resonant switch, and the simplified circuit and its steady state waveforms are shown in Fig.6. 17(b) and (c), respectively.

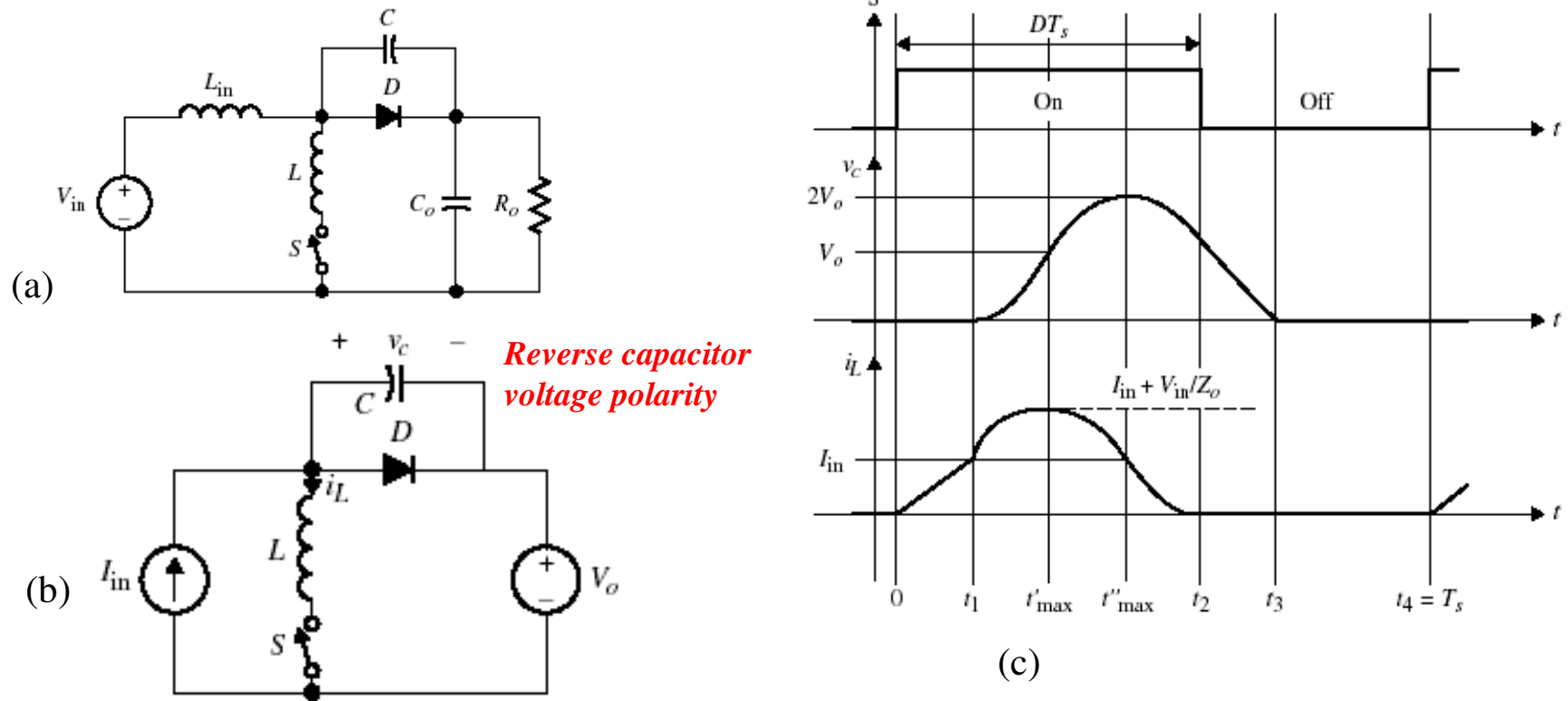

**Fig 6.17** (a) ZCS boost converter with L-type switch. (b) Simplified equivalent circuit. (c) Steady-state waveforms.