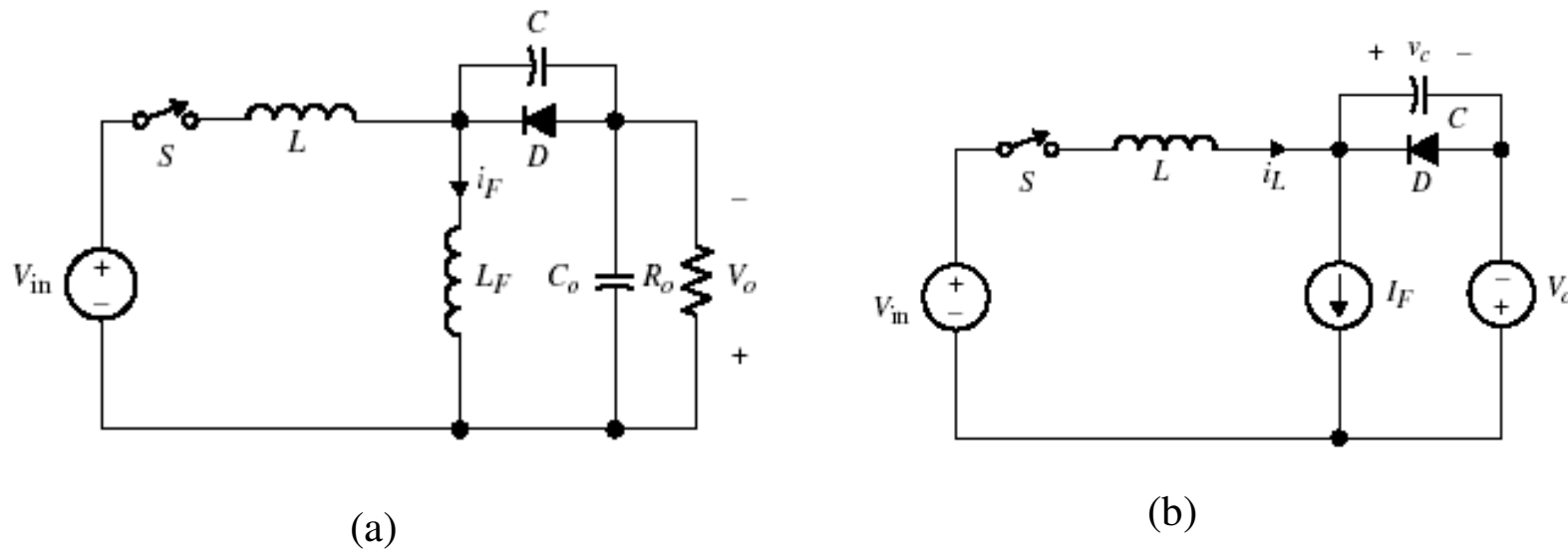


## ZCS Buck-boost Converter

Quasi-resonant buck-boost converter by using the L-type switch as shown in Fig. 6.18(a), Fig. 6.18(b) shows the simplified equivalent circuit.



**Fig 6.18** (a) ZCS buck-boost converter with L-type switch. (b) Simplified equivalent circuit.

## ZCS Buck-Boost Converter-Steady-State Analysis

### Mode I [ $0 \leq t < t_1$ ]:

Mode I starts at  $t = 0$ , the switch and the diode are both conducting. According to Kirchhoff's law, the voltage equation can be written as

$$L \frac{di_L(t)}{dt} = V_{in} + V_o \quad (6.50)$$

By integrating both sides of Eq. (6.50) with the initial condition of  $i_L(0) = 0$ , is given by,

$$i_L(t) = \frac{V_{in} + V_o}{L} t \quad (6.51)$$

and  $v_c(t) = 0$

At  $t = t_1$ , the inductor current reaches  $I_F$ , forcing the output diode to stop conducting, so  $t_1$  can be express as,

$$t_1 = \frac{LI_F}{V_{in} + V_o} \quad (6.52)$$

## Steady-State Analysis (cont'd)

### Mode II [ $t_1 \leq t < t_2$ ]:

This is a resonant stage between L and C with the initial conditions given by

$$v_c(t_1) = 0$$

$$i_L(t_1) = I_F$$

Applying Kirchhoff's law, in Fig. 6.19(b), the inductor current and capacitor voltage equations may be given as

$$L \frac{di_L}{dt} = V_{in} + V_o - v_c \quad (6.53a)$$

$$C \frac{dv_c}{dt} = i_L - I_F \quad (6.53b)$$

Solving Eqs. (6.53) for  $t > t_1$ ,

$$i_L(t) = I_F + \frac{V_{in} + V_o}{Z_o} \sin \omega_o(t - t_1) \quad (6.54)$$

$$v_c(t) = (V_{in} + V_o)[1 - \cos \omega_o(t - t_1)] \quad (6.55)$$

At  $t = t_2$ , the inductor current reaches zero,  $i_L(t_2) = 0$ , and the switch stops conducting. The time interval  $(t_2 - t_1)$  is given by,

$$(t_2 - t_1) = \frac{1}{\omega_o} \sin^{-1} \left( -\frac{I_F Z_o}{V_{in} + V_o} \right) \quad (6.56)$$

## Steady-State Analysis (cont'd)

### Mode III [ $t_2 \leq t < t_3$ ]:

Mode III starts at  $t = t_2$  when the inductor current reaches zero. The switch and the diode are both *OFF*. The capacitor starts to discharge until it reaches zero, and the diode will start to conduct again at  $t = t_3$ . During this period, the inductor current is zero.

$$v_c = \frac{-1}{C} \int_{t_2}^t I_F dt = \frac{-I_F}{C} (t - t_2) + v_c(t_2)$$

The diode begins to conduct at the end of this mode,  $t = t_3$ , because the capacitor voltage is equal to zero

$$0 = \frac{-I_F}{C} (t_3 - t_2) + v_c(t_2)$$


where  $v_c(t_2)$  may be obtained from Eq. (6.55) by evaluating it at  $t = t_2$ . The expression from Eq. (6.57) for the time between  $t_2$  and  $t_3$  is,

$$(t_3 - t_2) = \frac{C}{I_F} v_c(t_2)$$

### Mode IV [ $t_3 \leq t < t_4$ ]:

Between  $t_3$  and  $t_4$ , the switch remains *OFF*, but the diode is *ON*. At the end of the cycle, the switch is closed again when the current is zero. The cycle of the modes will repeat again at  $T_s$ .


## ZCS Buck-Boost Converter-Equivalent Circuit Modes

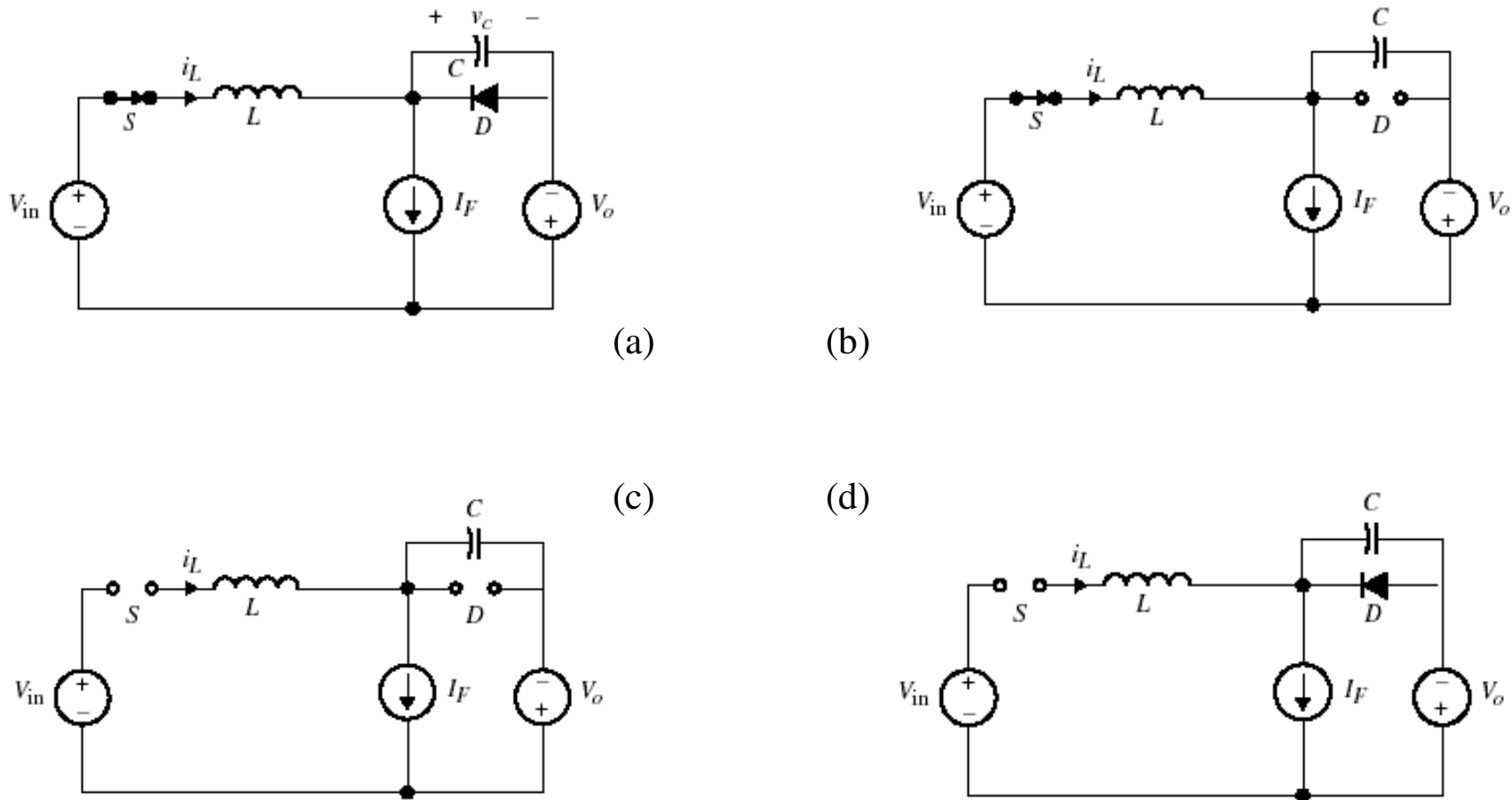

**Fig 6.19** (a) Equivalent circuit for mode I. (b) Equivalent circuit for mode II. (c) Equivalent circuit for mode III. (d) Equivalent circuit for mode IV.

## ZCS Buck-Boost Converter – Typical Steady-State Analysis

The steady state waveforms shown in Fig. 6.20 are the characteristic waveforms for the switch,  $v_c$ , and  $i_L$ .

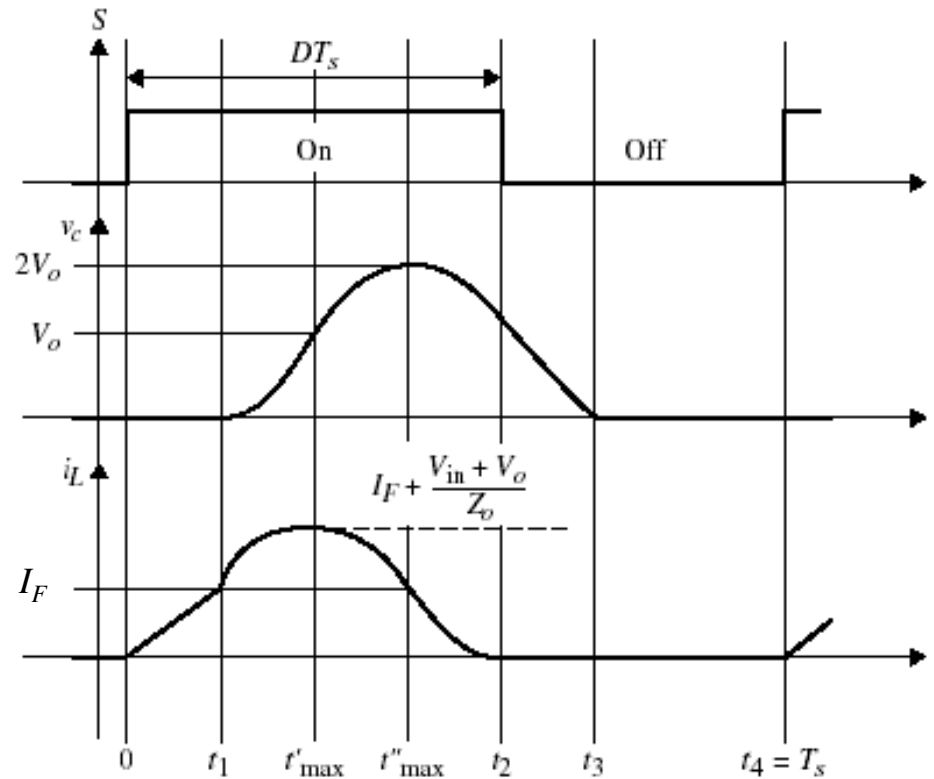

**Fig 6.20** Steady-state waveforms for buck-boost converter with L-type switch.

## ZCS Buck-Boost Converter


### Voltage Gain

- Conservation of energy per switching cycle will be used as before to obtain the voltage gain,

$$M = V_o / V_{in}$$

- The buck-boost-ZCS converter gain is given by

$$\frac{M}{1+M} = \frac{f_{ns}}{2\pi} \left\{ \frac{M}{2Q} + \alpha + \frac{Q}{M} [1 - \cos(\alpha)] \right\} \quad (6.59)$$

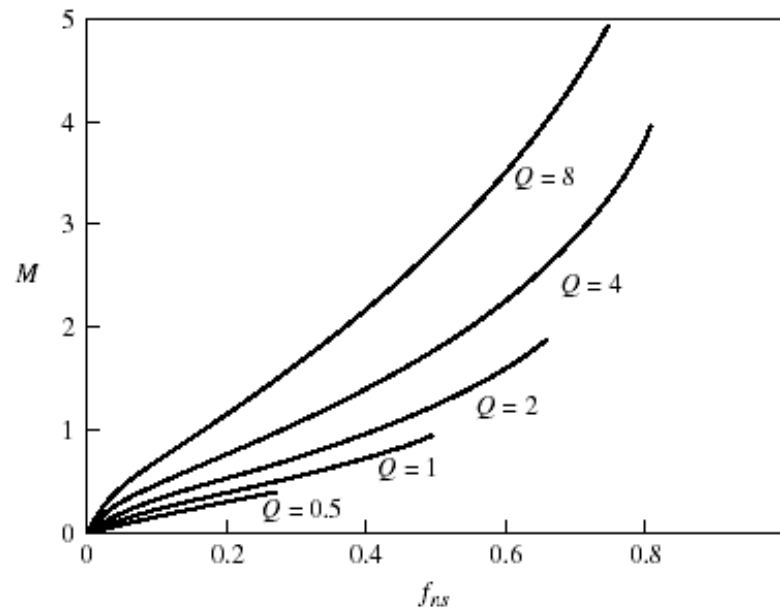

**Fig 6.21** Characteristic curve for  $M$  vs.  $f_{ns}$  for the ZCS buck-boost converter.

### Example 6.4

Consider a buck-boost QRC-ZCS converter with the following specifications:

$V_{in}=40V$ ,  $P_o=80W$  at  $I_o=4A$ ,  $f_s=250kHz$ ,  $L_o=0.1mH$ , and  $C_o=6\ \mu F$ . Design values for L and C and determine the output ripple voltage.

#### Solution:

The output voltage and load resistance are given by

$$V_o = \frac{80}{4} = 20V \quad R_o = \frac{20}{4} = 5\Omega$$

The voltage gain is given by

$$\frac{V_o}{V_{in}} = \frac{20}{40} = 0.5$$

With  $M = 0.5$ , and  $f_{ns} = 0.17$ , we select,  $Q = 3$  to yield,  $f_o = \frac{250}{0.17} = 1470.6kHz$

From Q, and  $Z_o$ ,

$$Q = \frac{R_o}{Z_o} = \frac{5}{Z_o} \quad Z_o = \frac{3}{5} = 0.6\Omega \quad \sqrt{L/C} = 0.6$$

and

$$\sqrt{1/LC} = 2\pi f_o = 2\pi \times 1470.6 \times 10^3 \quad \frac{1}{C} = 0.6 \times 2\pi \times 1470.6 \times 10^3$$

From the above equation C and L are given by,

$$C = 180.4nF \quad L = 3^2 \times C = 1.6\mu H$$

The duty cycle D is approximately 33% since the voltage gain for the buck-boost is 0.5. Hence, the voltage ripple is,

$$\frac{\Delta V_o}{V_o} = \frac{D}{RC_o f} = \frac{0.5}{5 \times 6 \times 10^{-6} \times 250 \times 10^3} = 6.67\%$$