

## **Zero-voltage and Zero-current Transition Converter**

- Traditional converters operate with a sinusoidal current through the power switches, which results in high peak and rms currents for the power transistors and high voltage stresses on the rectifier diodes.
- When the line voltage or load current varies over a wide range, Quasi-Resonant Converters are modulated with a wide switching frequency range, making the circuit design difficult to optimize.
- As a compromise between the PWM and resonant techniques, various soft-switching PWM converter techniques proposed to aim at combining desirable features of both the conventional PWM and Quasi-Resonant techniques without a significant increase in the circulating energy.


## Switching Transition

- To overcome the limitations of the quasi-resonant converters, zero-voltage transition (ZVT) or zero-current transition (ZCT) is the solution. Instead of using a series resonant network across the power switch, a shunt resonant network is used across the power switch.
- The features of the ZCT PWM and ZVT PWM soft-switching converters are summarized as follows:
  - Zero-current/voltage turn-off/on for the power switch
  - Low voltage/current stresses of the power switch and rectifier diode
  - Minimal circulating energy
  - Constant-frequency operation
  - Soft switching for a wide line and load range
- One disadvantage is that the auxiliary switch does not operate with soft switching; it is hard-switching, but the switching loss is much lower than that of a PWM converter.

## ZVT & ZCT Switch

The ZVT and ZCT converters differ from the conventional PWM converters by the introduction of a resonant branch.


Figure 6.48(a) shows the ZVT-PWM switching cell

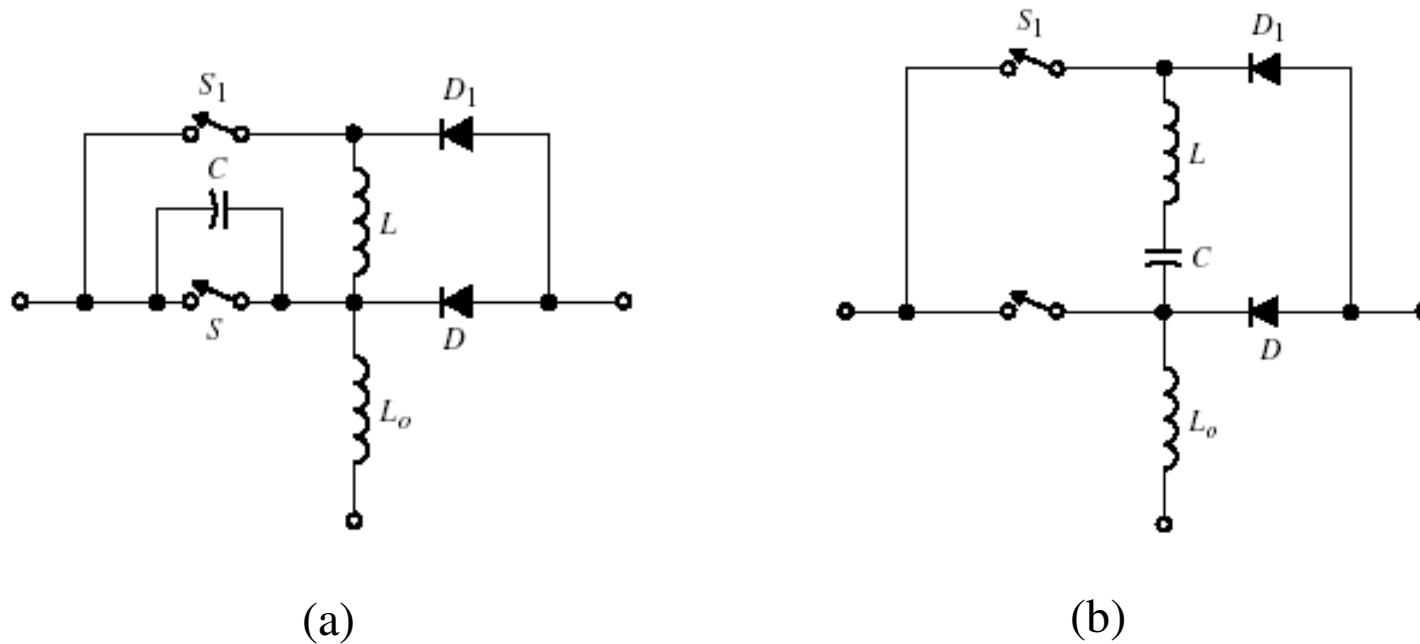

**Fig 6.48** (a) ZVT PWM switching cell. (b) ZCT PWM switching cell.


## The Boost ZVT PWM Converter

- The boost ZVT PWM, shown in Fig. 6.49, by placing the ZVT PWM switching cell shown in Fig. 6.48(a) into the conventional boost converter.

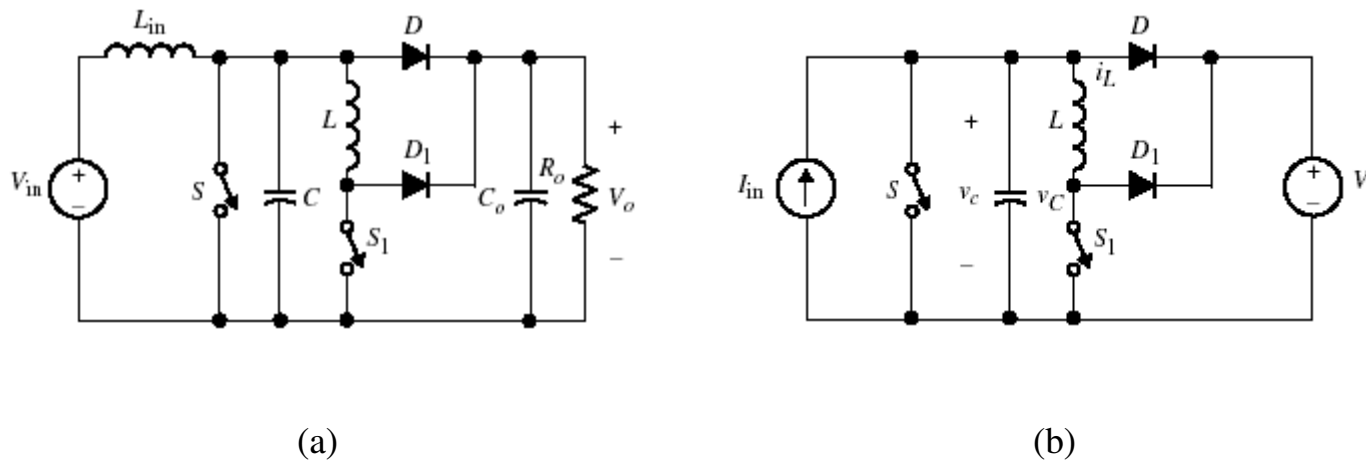


**Fig 6.49** (a) Boost ZVT PWM. (b) Simplified equivalent circuit.

The switching cycle is divided into six modes

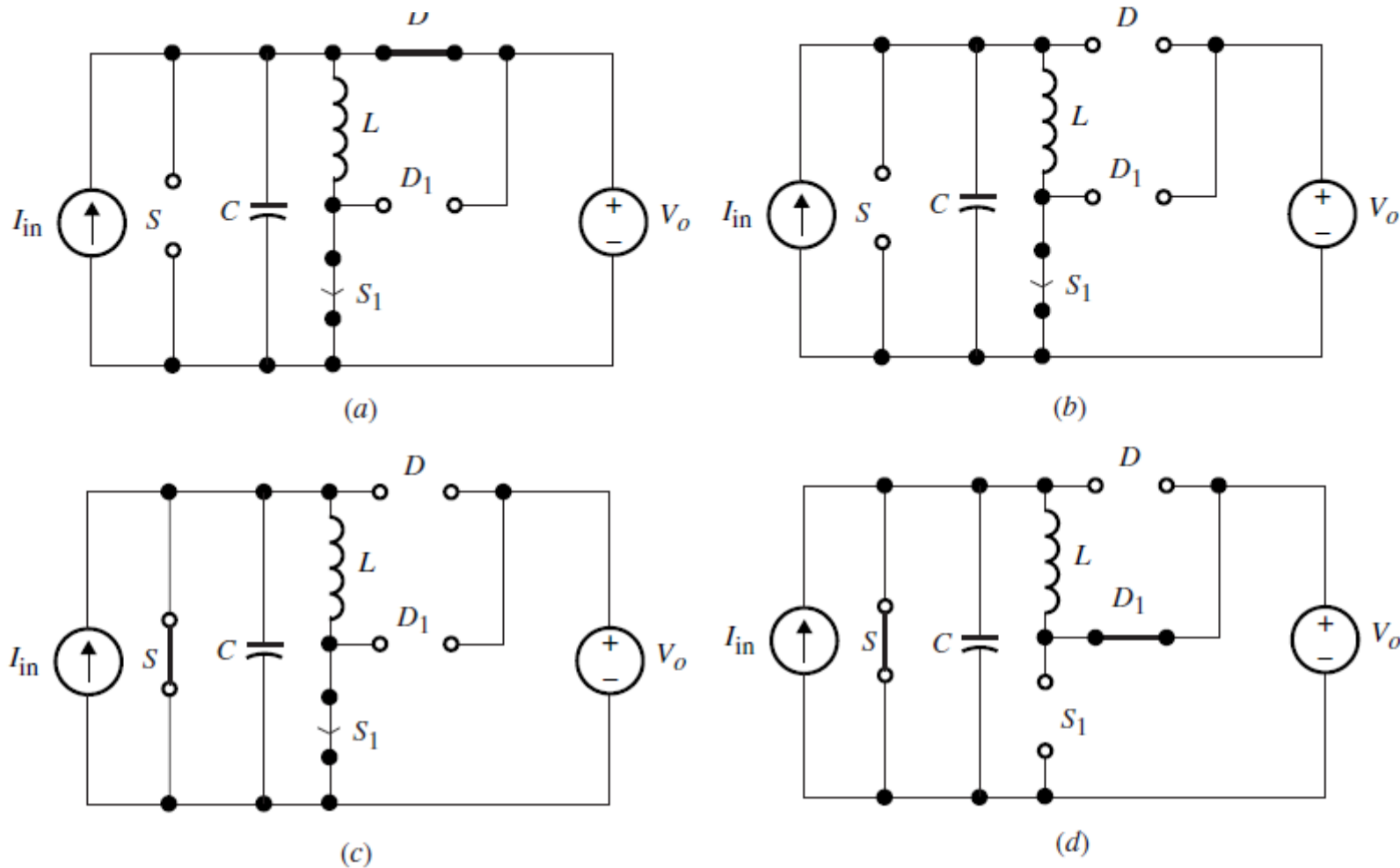

**Figure 6.50** Equivalent circuits for the six modes of operation: (a) mode I, (b) mode II, (c) mode III, (d) mode IV, (e) mode V, and (f) mode VI.

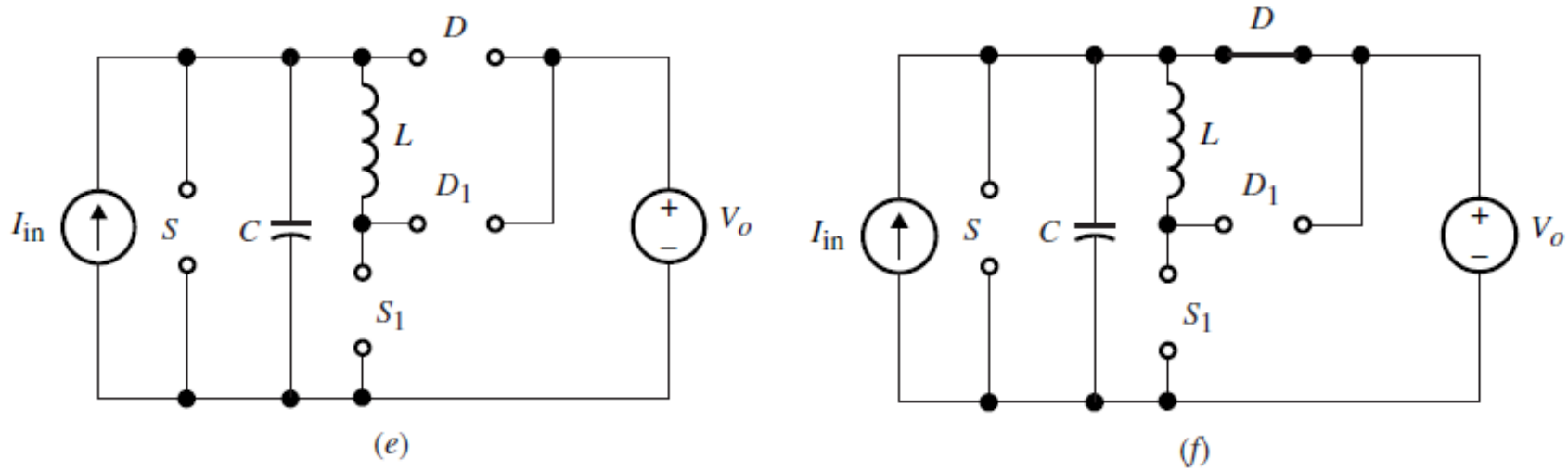

**Figure 6.50** Equivalent circuits for the six modes of operation: (a) mode I, (b) mode II, (c) mode III, (d) mode IV, (e) mode V, and (f) mode VI.

## Steady State Analysis

### Mode I [ $t_0 \leq t < t_1$ ]

- Mode I starts at  $t = t_0$  when the auxiliary switch  $S_1$  is turned *ON*.
- Since the main switch,  $S$ , and the auxiliary switch  $S_1$  were *OFF* prior to  $t = t_0$ ,
- The capacitor voltage  $v_c$  is equal to the output voltage  $V_o$  and also equal to the inductor voltage as given by,

$$V_o = L \frac{di_l}{dt} = v_c$$

The inductor current  $i_l$  is given by,

$$i_l = \frac{V_o}{L} (t - t_0)$$

The above equation assumes zero initial condition for  $i_l$

## Steady State Analysis (cont'd)

As long as the inductor current is less than  $I_{in}$ , the diode will stay conducting and the capacitor voltage remains at  $V_o$ . At time  $t_1$ , the inductor current becomes equal to  $I_{in}$ , D stops conducting, and the circuit enters Mode II. From the above equation, we have,

$$I_{in} = \frac{V_o}{L}(t - t_0)$$

The time interval is given by

$$(t_1 - t_0) = \frac{L I_{in}}{V_o}$$

This is the inductor current charging state.

### Mode II [ $t_1 \leq t < t_2$ ]

Mode II starts at  $t_1$  when D is *OFF*, resulting in a resonant stage between  $L$  and  $C$ . During the time between  $t_1$  and  $t_2$ , the main switch, remains *OFF*, and  $S_1$  is still *ON*, but  $S_2$  both diodes are *OFF*. The initial capacitor voltage is still  $V_o$ , but the initial  $I_{in}$  has changed to  $I_{in}$ . The first order differential equations that represent this mode are given by,

$$C \frac{dv_c}{dt} = I_{in} - i_L$$

$$v_c(t) = L \frac{di_L}{dt}$$



## Steady State Analysis (cont'd)

Equation (6.109) is obtained from the above two equations.

$$\frac{d^2 i_L}{dt^2} - \frac{1}{LC} i_L = \frac{1}{LC} I_{in}$$

The solution for  $i_L$  and  $v_c$  is given by,

$$i_L = \frac{V_o}{Z} \sin \omega_o(t - t_1) + I_{in}$$

$$v_c = V_o(2 - \cos \omega_o(t - t_1))$$

The time interval between  $t_1$  and  $t_2$  is given by

$$(t_2 - t_1) = \frac{1}{\omega_o} \cos^{-1}(2)$$

The diode voltage starts to charge up due to the decreasing capacitor voltage.

$$v_d = V_o - v_c$$

Substituting for  $v_c$ , the diode voltage becomes,

$$v_d(t) = -V_o + V_o \cos \omega_o(t - t_1)$$

## Steady State Analysis (cont'd)

### Mode III [ $t_2 \leq t < t_3$ ]:

Mode III starts when the capacitor discharge to zero. In this mode the main switch, S remains *OFF*, the auxiliary switch,  $S_1$  is still *ON*, and both diodes are *OFF*.

The switch anti-parallel diode () start conducting in this mode.

$$v_c(t) = 0$$

### Mode IV [ $t_3 \leq t < t_4$ ]:

Mode IV starts at  $t = t_3$ , when the main switch, S is turned *ON* and the auxiliary switch,  $S_1$  is turned *OFF*. At  $t_3$ , the initial capacitor voltage is zero, and the inductor starts linearly discharging from  $i_L(t_2)$  to zero during  $t_3$  to  $t_4$ . The diode D remain *OFF* since its voltage is negative, but  $D_1$  turns *ON* at  $t = t_3$  to carry the inductor current.

The input voltage is equal to the inductor voltage, and the output voltage is equal to the negative of inductor voltage,  $v_L$

$$v_L = L \frac{di_L}{dt} = -V_o$$

The inductor current for  $t > t_2$ , is given by,

$$i_L(t) = -\frac{V_o}{L}(t - t_2) + i_L(t_2)$$

## Steady State Analysis (cont'd)

### Mode V [ $t_4 \leq t < t_5$ ]:

In this mode, at  $t = t_4$  both switches are *OFF*, and also both diodes are *OFF*. The inductor current is zero, and the input current is only going through the capacitor,

$$I_{in} = C \frac{dv_c}{dt}$$

The capacitor voltage can be expressed as,

$$v_c(t) = \frac{1}{C} I_{in} (t - t_4)$$

The capacitor is charging up from zero and will reach the output voltage at  $t = t_5$

The time interval is,


$$(t_5 - t_4) = \frac{V_o C}{I_{in}}$$

then it enters mode VI at this point.

### Mode VI [ $t_5 \leq t < t_6$ ]

When the capacitor reaches the output voltage, D starts conducting, but in this mode, both switches are still *OFF*. The diode current will equal the input current immediately. At  $t = t_5$ , the capacitor voltage is equal to the output voltage until the auxiliary switch is turned *ON* again, then the cycle will repeat from mode I. The waveforms for the six modes of operation are shown in Fig.6.51.

## Steady State Waveforms

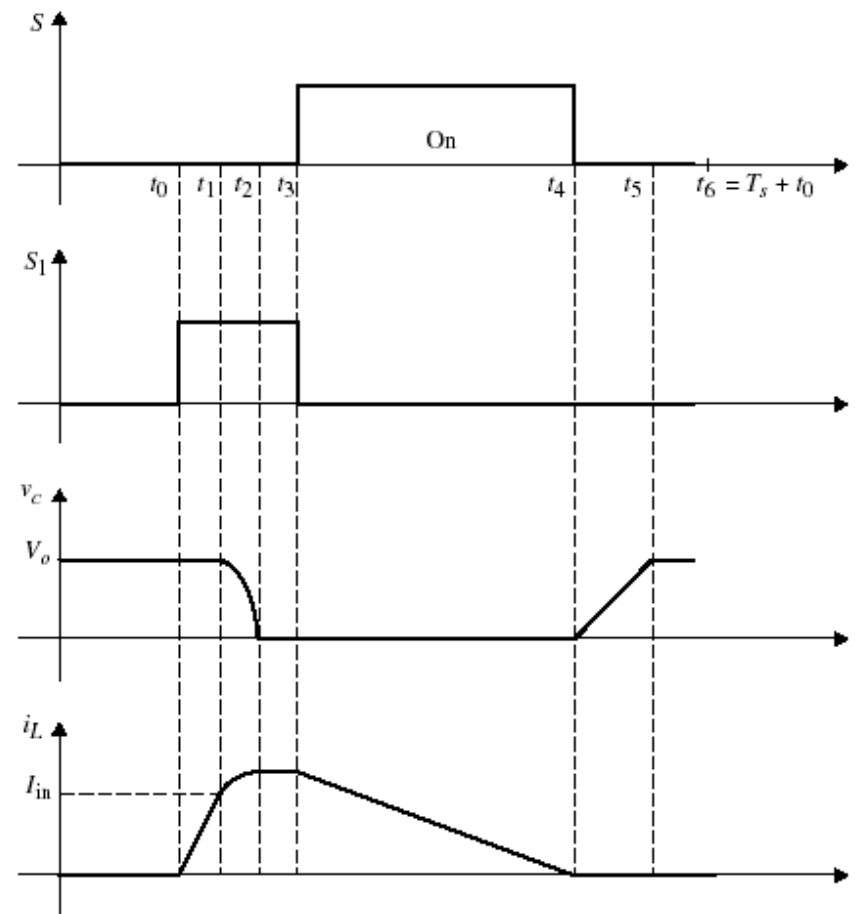

**Fig 6.51** Steady-state waveforms for the ZVT boost converter of Fig 6.49(b).