



EEL 5245 POWER ELECTRONICS I
Lecture #13: Chapter 4
Non-Isolated DC-DC Converters
PWM Converters
Boost and Buck Boost Analysis (CCM)



Objectives

- **Boost and Buck-Boost Converter Analysis (CCM)**
 - **Voltage Conversion Ratio (M =Gain)**
 - **Average Input and Output Currents**
 - **Output Voltage Ripple via Charge approximation**
 - **Boundary Between CCM and DCM**
- **iPES Examples for Boost CCM**
- **Calculation Example**
- **Analysis Verification by Simulation**




Figures of Merit for the PWM DC-DC Converter “Plan of Attack”

- **Classic Converter Analysis (CCM)**
 - **Voltage Conversion Ratio (M=Gain)**
 - Use Inductor Volt-second balance
 - **Average Input and Output Currents**
 - Use waveform analysis and
 - Capacitor charge balance and small ripple approximation ($I_{cav} = 0$)
 - **Output Voltage Ripple via Charge approximation**
 - Small ripple approximation means all ac component of output current seen by capacitor, DC to load R
 - **Inductor current Ripple**
 - Derived from inductor current waveform
 - **Boundary Between CCM and DCM**
 - Concept of Critical Inductance derived from i_L expressions




Boost Converter Analysis (Step Up)

*Boost Converter
w/ Ideal Switch*

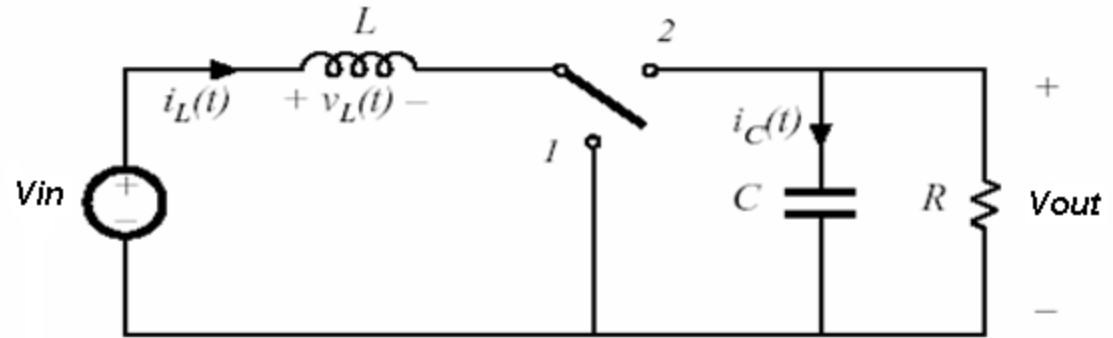


*Boost Converter
realized w/
MOSFET*

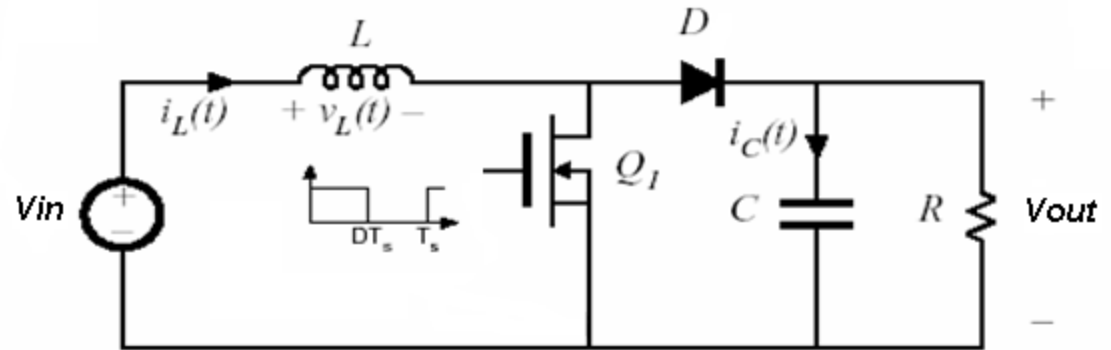



Boost Converter Analysis



Circuit Modes

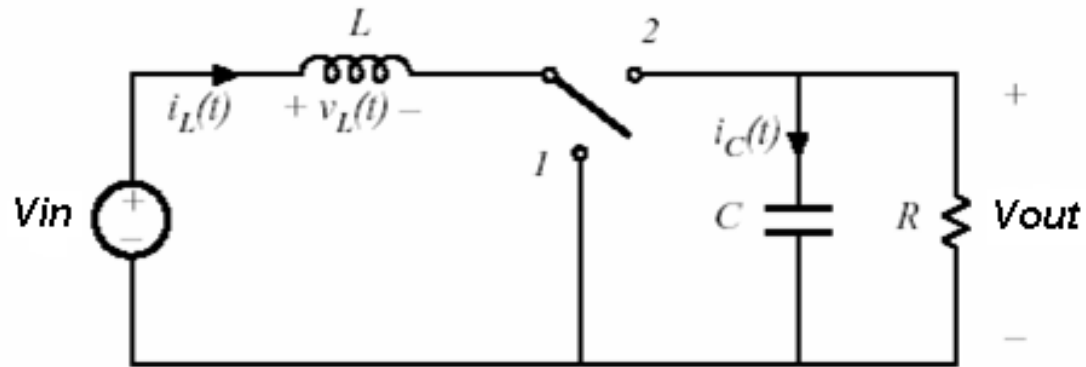

Position 1



Position 2

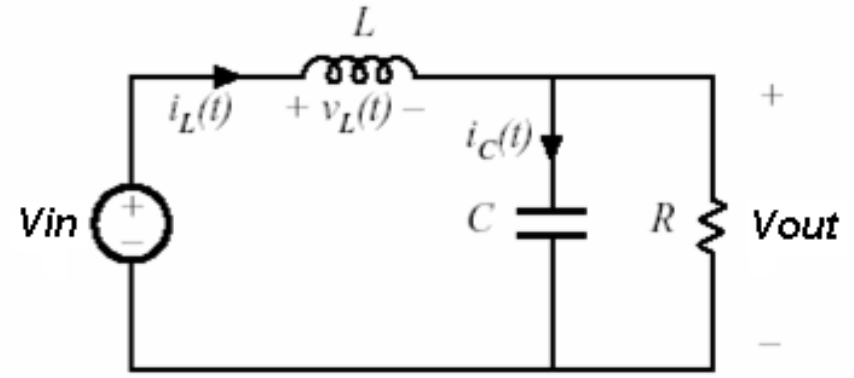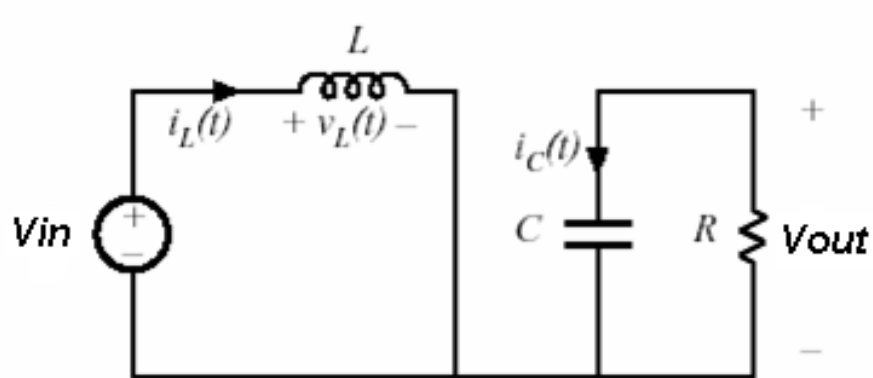




Boost Converter Analysis Circuit Mode I

**Inductor Voltage and
Capacitor Current**

$$v_L = V_{in}$$

$$i_c = -\frac{V_{out}}{R}$$

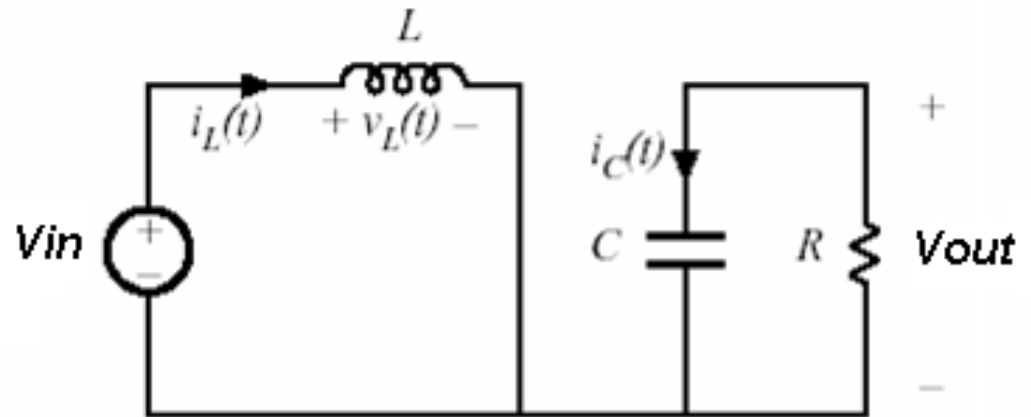




Boost Converter Analysis

Circuit Mode II

**Inductor Voltage and
Capacitor Current**

$$v_L = V_{in} - V_{out}$$





$$i_c = I_L - \frac{V_{out}}{R}$$

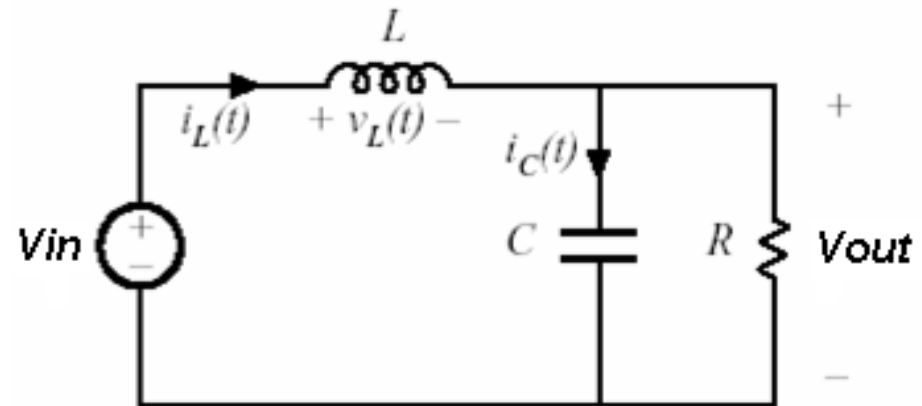



Boost Converter Analysis

Inductor Voltage and Capacitor Current

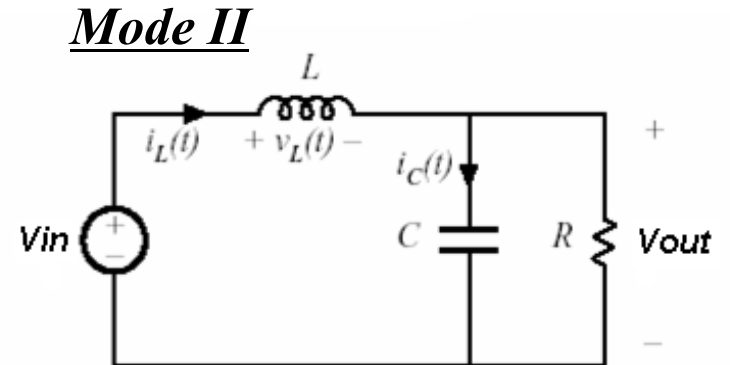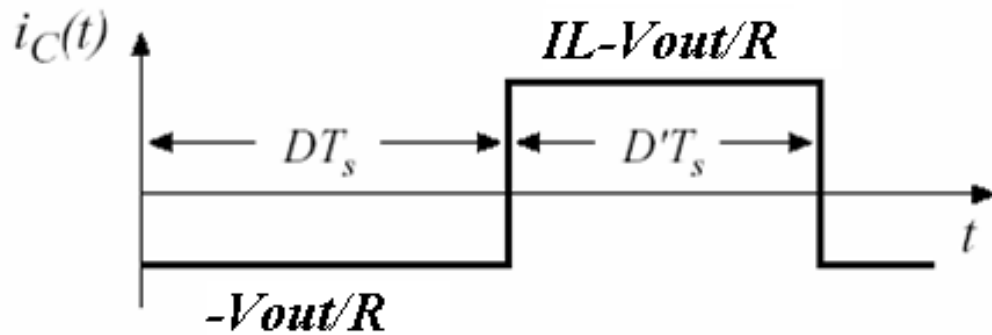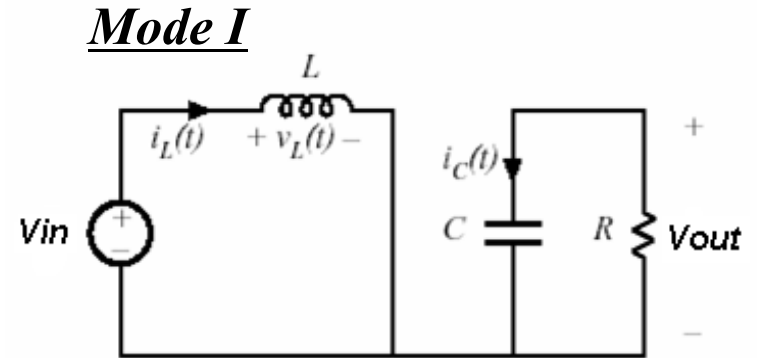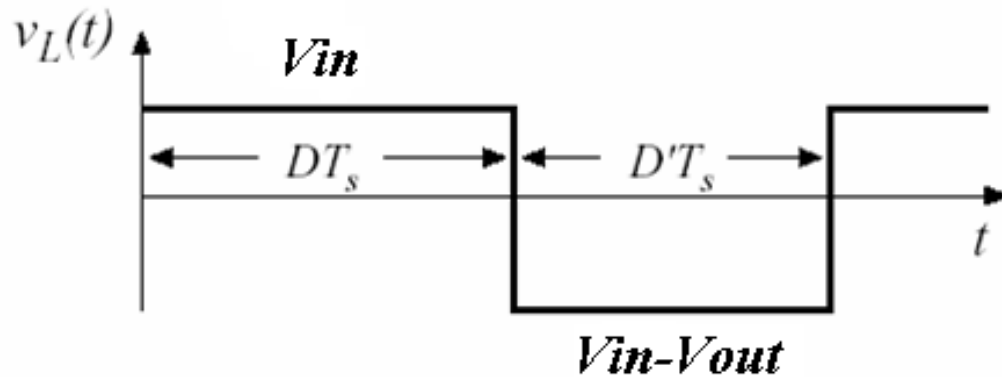




Boost Converter Analysis

Inductor Voltage Second Balance

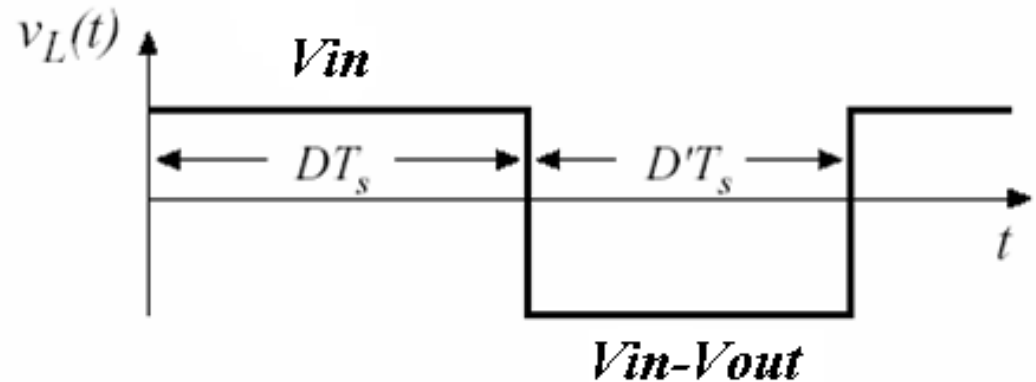Net volt-seconds applied to inductor over one switching period:



$$\int_0^{T_s} v_L(t) \cdot dt = V_{in} \cdot D \cdot T_s + (V_{in} - V_{out}) \cdot (1 - D) \cdot T_s$$



Set equal to zero and solve:

$$V_{in} \cdot (D + 1 - D) - V_{out} \cdot (1 - D) = 0 \quad \Longrightarrow \quad M(D) = \frac{V_{out}}{V_{in}} = \frac{1}{1 - D}$$



Boost Converter Analysis


Voltage Conversion Ratio

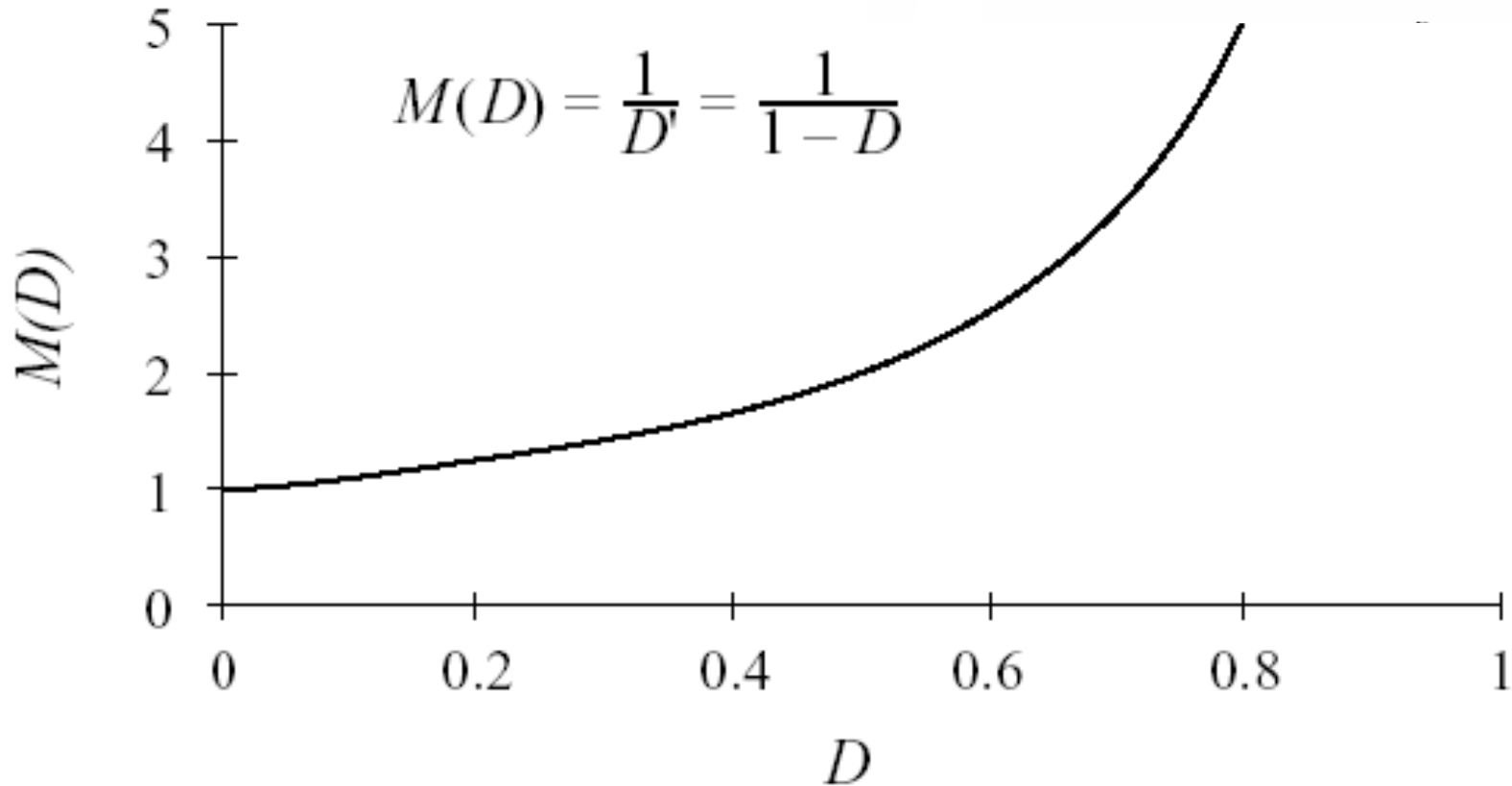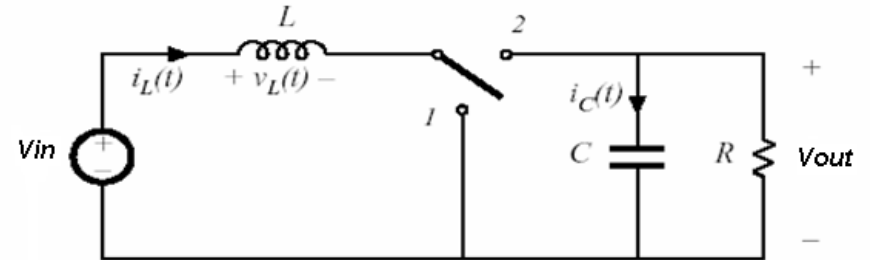



Boost Converter Analysis

Capacitor Current Average Value

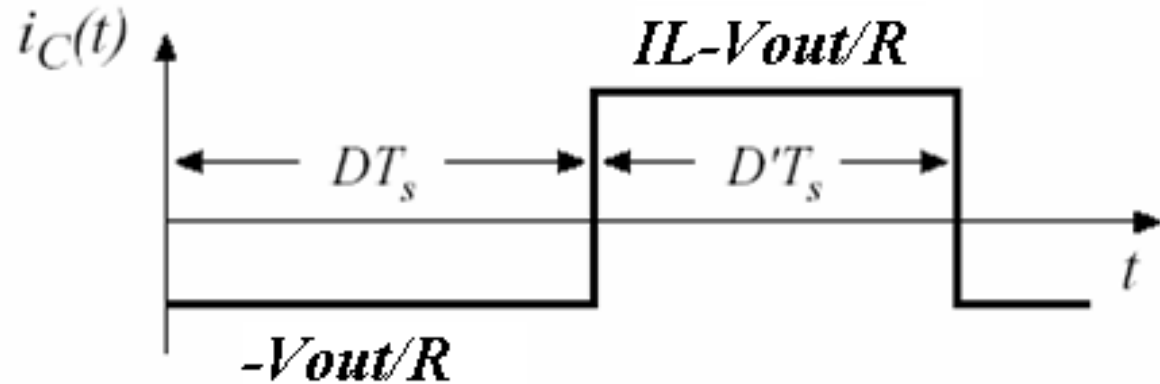

Capacitor charge balance:

$$\int_0^{T_s} i_c(t) \cdot dt = \left(-\frac{V_{out}}{R}\right) \cdot D \cdot T_s + \left(I_L - \frac{V_{out}}{R}\right) \cdot (1-D) \cdot T_s = 0$$


Set equal to zero and solve:

$$-\frac{V_{out}}{R} \cdot (D + 1 - D) + I_L \cdot (1-D) \cdot T = 0_s \quad \Longrightarrow \quad I_L = I_{in} = \frac{V_{in}}{(1-D)^2 \cdot R}$$



Boost Converter Analysis

Inductor Current Ripple

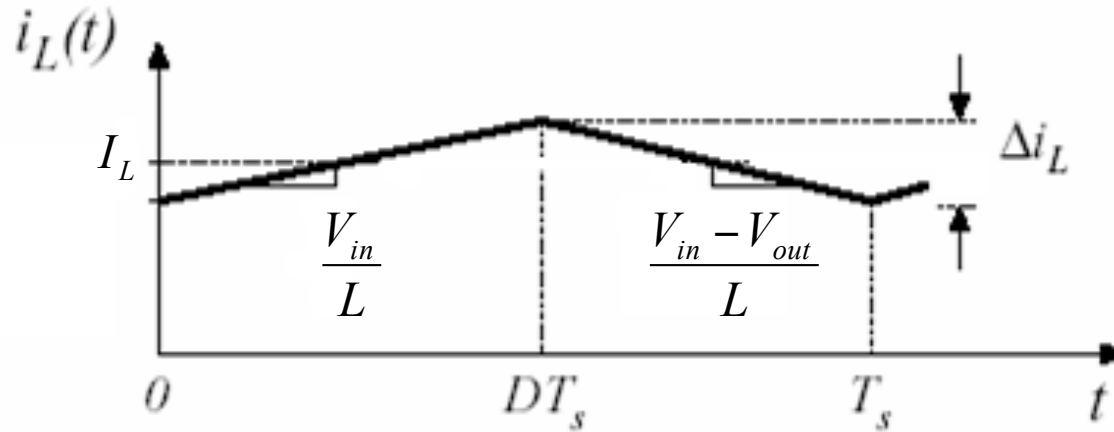


Change in inductor current during Mode I = Change in inductor current during Mode II (assuming steady-state)

$$\Delta i_L = \frac{V_{in}}{L} \cdot D \cdot T_s = \frac{V_{in} - V_o}{L} \cdot (1 - D) \cdot T_s$$



Boost Converter Analysis

Capacitor Voltage Ripple

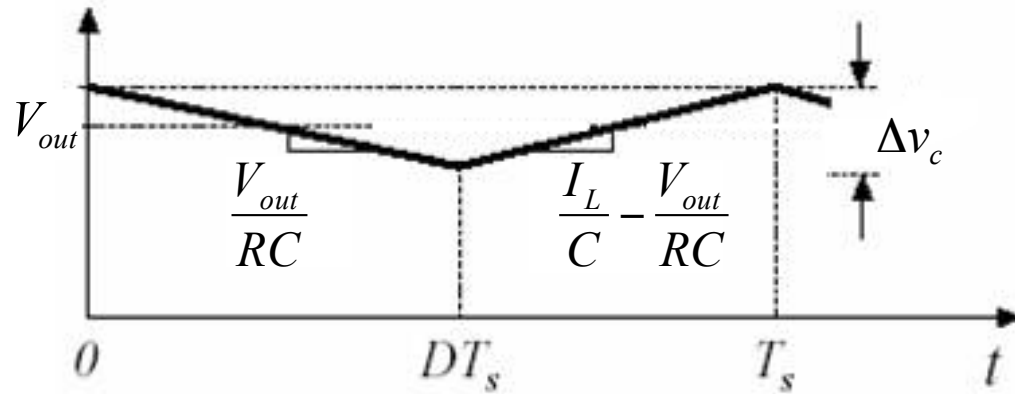

Change in capacitor voltage during Mode I = Change in capacitor voltage during Mode II (assuming steady-state)

$$\Delta v_c = \frac{V_{out}}{RC} \cdot D \cdot T_s$$



Boost Converter Analysis: iPES Examples for Boost CCM

DC/DC-Converter Basic Topologies

Boost-Converter

Boost-Converter: Start-Up with Constant Duty Cycle



Boost Converter Analysis

Hand Calculation Example 4.4

Example 4.4:

Sketch the current waveforms for $i_L, i_{in}, i_D, i_o, i_c$ for the boost converter with the following parameters: $L=1.8\text{mH}, V_{in}=50\text{V}, V_o=120\text{V}, R=20\Omega, C=147\mu\text{F}$, and $f=15\text{kHz}$.

Also sketch the voltage waveform v_L, v_{switch}, v_c and v_D .



Boost Converter Analysis: Hand Calculation Example 4.4

Example 4.4

Sketch all waveforms for a boost converter with the following circuit parameters: $V_{in} = 50\text{V}$, $V_o = 120\text{V}$ and $R = 20$, $f_s = 15\text{kHz}$
 $L = 1.8\text{mH}$, $C = 147\mu\text{F}$

Solution:

In order to sketch the waveforms, we need to find D , the maximum and minimum inductor currents, and the average output current.

The duty cycle is given by,

$$\frac{V_o}{V_{in}} = \frac{1}{1-D} = \frac{120}{50}$$

Yields, $D = 0.58$



Boost Converter Analysis: Hand Calculation Example 4.4

Using $R=20\Omega$ and $T=66.67\mu s$, the maximum and minimum inductor currents are given by,

$$I_{Lmax} = V_{in} \left(\frac{1}{(1-D)^2 R} + \frac{DT}{2L} \right) = 14.71A \quad I_{lmax}=14.937$$

and,

$$I_{Lmin} = V_{in} \left(\frac{1}{(1-D)^2 R} - \frac{DT}{2L} \right) = 13.635A \quad I_{lmin}=13.863$$

The average input and output currents are given by,

$$I_{in} = \frac{I_{Lmax} + I_{Lmin}}{2} = 14.17A \quad I_{inavg}=14.4$$

$$I_o = I_{in}(1-D) = 5.95A \quad I_{oavg}=6$$



Boost Converter Analysis:

Hand Calculation Example 4.4

$$I_{c\max} = I_{L\max} - I_o = 8.76 A$$

$$I_{c\max} = 14.937 - 6 = 8.937$$

$$I_{c\min} = I_{L\min} - I_o = 7.685 A$$

Hence,

$$\Delta I_c = I_{c\max} - I_{c\min} = 1.01 A$$

$$I_{c\min} = 13.863 - 6 = 7.863$$

Notice this value must be equal to ΔI_L .

The capacitor voltage is given by,

$$v_c(t)|_{t=0} = 120V$$

$$\Delta I_c = 1.074$$

$$v_c(t)|_{t=DT} = \frac{-I_o}{C} DT + 120V$$

$$\begin{aligned} \text{Ripple} &= D / (R * C * f) = 1.32\% \\ &= 1.58V \end{aligned}$$


$$= \frac{-5.95A}{147\mu F} (0.58)(66.67\mu s) + 120V = 118.43V$$

Hence, the ripple is 1.57 volts




Boost Converter Analysis: Simulation Verification

Example 4.4

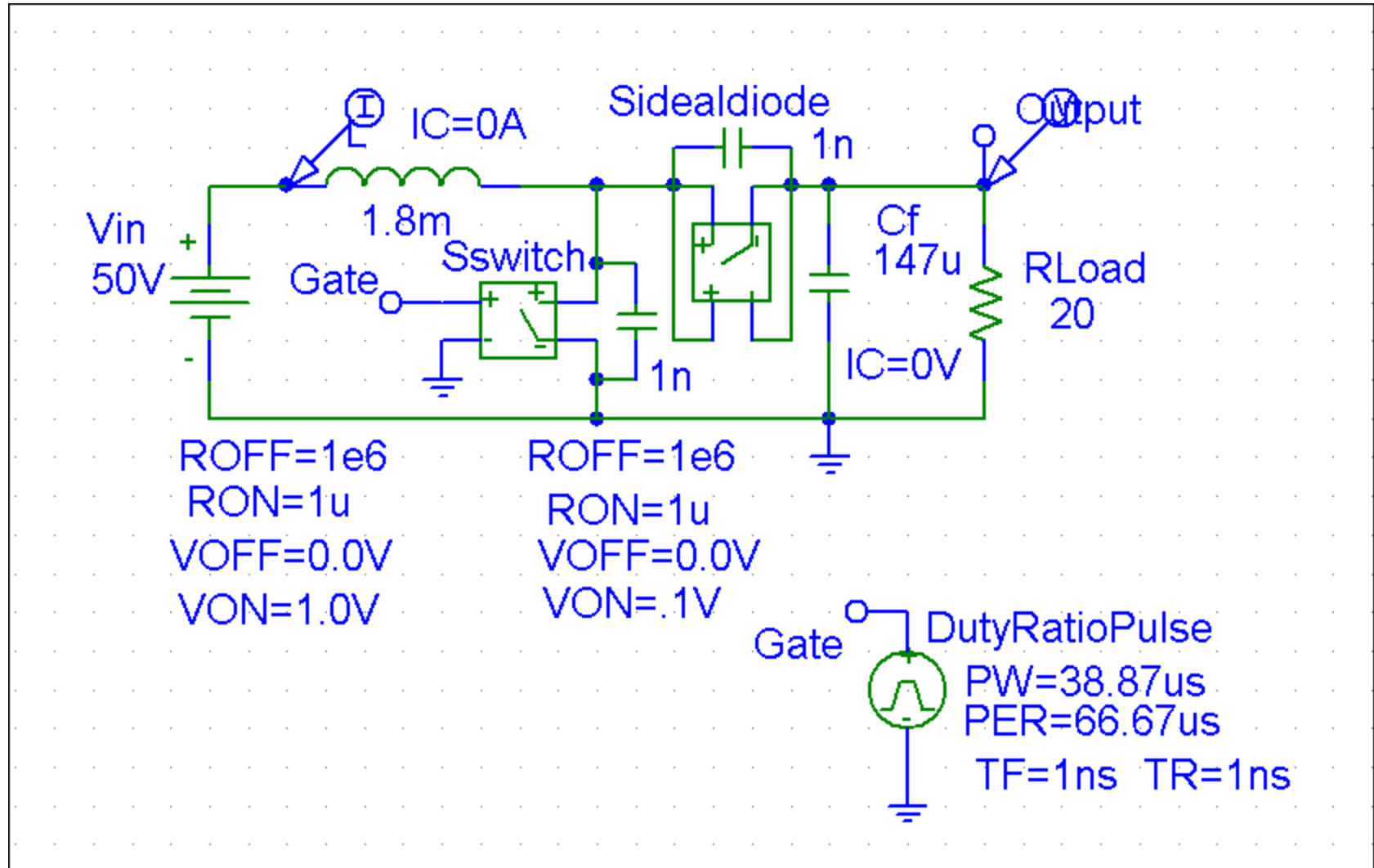




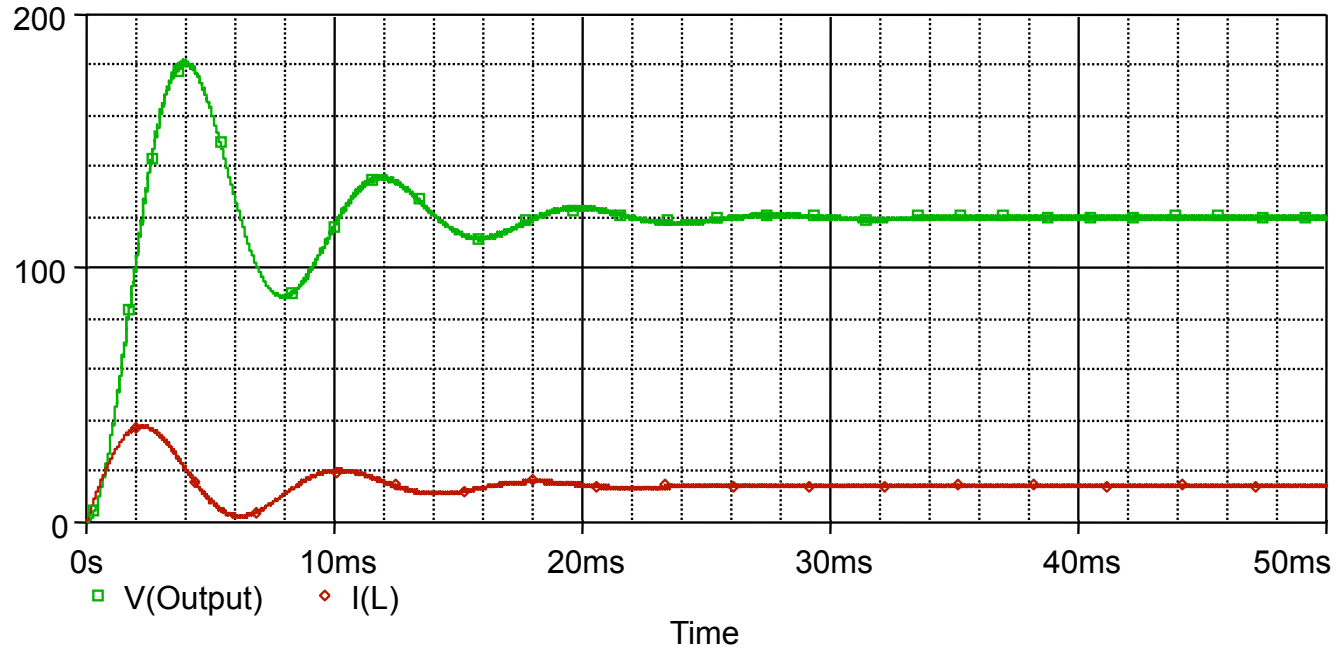
Boost Converter Analysis: Simulation Verification Example 4.4-Startup





Boost Converter Analysis: Simulation Verification

Example 4.4-Inductor Current/Voltage

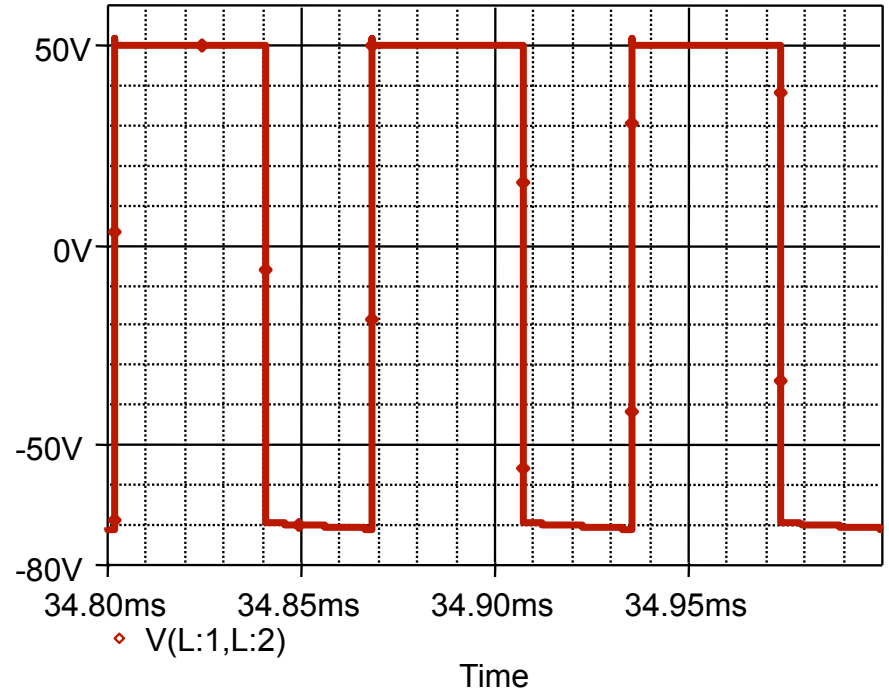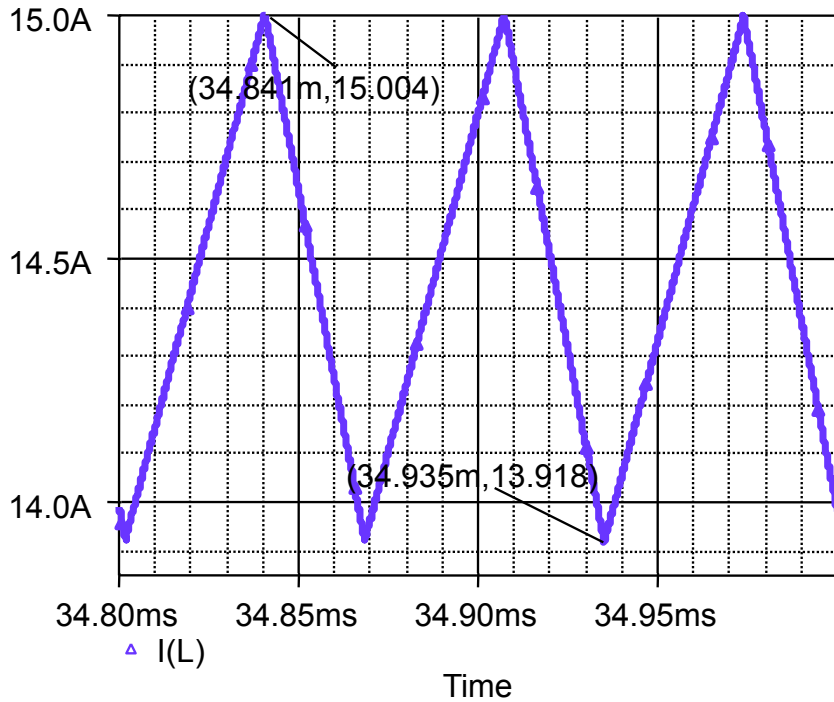



Boost Converter Analysis: Simulation Verification

Example 4.4-Capacitor Current/Voltage

